

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE and ECE.

Semester : 1st

Title of the Course : Introduction to Electrical &
Electronics Engineering

Course Code : EEB100

Time: 2 Hours

Maximum Marks: 25

- Note :** 1. This paper contains 7 questions in 2 printed pages.
2. Answer all the questions.

1. For the circuit shown in Fig.1, use nodal analysis to determine V_x and V_s . What is the power consumed by the $6\ \Omega$ resistance? Also calculate the power supplied by $240\ V$ and $60\ V$ voltage sources. [4]

 


Fig. 1

2. Obtain the Thevenin's and Norton's equivalent circuit across $x - y$ terminals shown in Fig.2. [4]

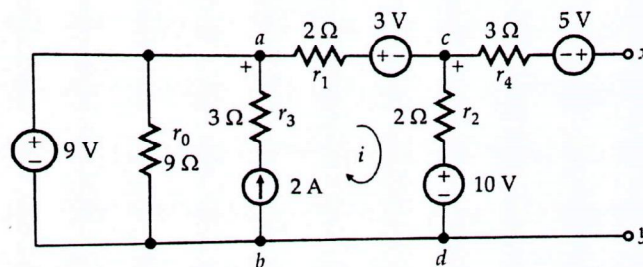


Fig. 2

3. In a series RLC circuit, the maximum inductor voltage is twice the capacitor voltage maximum. However, the circuit current lags the applied voltage by 30° and the instantaneous drop across the inductance is given by $v_L = 100 \sin 377t \text{ V}$. Assuming the resistance being 20Ω , find the values of the inductance and capacitance. [4]

4. a) Subtract 14 from 46 using 8-bit 2's complement arithmetic.
 b) Convert $(5497)_{10}$ to radix 8 number system.
 c) Convert $(A0F9.0EB)_{16}$ to decimal number system.
 d) Convert $(756.603)_8$ to hexadecimal number system.
 e) Construct a truth table for the expression $f = \bar{x}y + yz + xz$
 f) Express the following Boolean function in a standard POS form.

$$f = AB + \bar{A}C$$

[1*6]

5. Design the following function using basic logic gates and also reduce the function using Boolean algebra rules and then redesign the reduced function using NAND gates only.

$$f = A[B + \bar{C}(AB + A\bar{C})]$$

[2]

6. Simplify the following expression and design it using 2-input NAND gates only.

$$f = A\bar{B} + ABD + AB\bar{D} + \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C}$$

[2]

7. Draw the input (J and K) and output (Q and Q') waveform of the J-K flip shown in fig. 3 for the 6 consecutive clock pulses. Assume that the one of the input of the AND gate follows a sequence 110101 at negative edge of clock pulse. Initially flip flop is in reset state i.e. $Q=0$ and $Q'=1$.

 


Fig. 3

[3]