

Roll No.:.....

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : 5

Title of the Course : Power System Analysis

Course Code : EEL 302

Time: 10:00-12:00noon

Maximum Marks: 25

Note: Attempt all questions.

- | | Mark |
|---|------|
| Q. [1] State the advantages of per unit (p. u.) system. | 2 |
| Q. [2] What are the different types of buses in power systems? What are the quantities specified at each bus? | 2 |
| Q. [3] If the reactance in ohms is 15 ohms, find the p. u. value for a base of 15 KVA and 10 KV. | 2 |
| Q. [4] A single-phase two winding transformer is rated 20 kVA, 480/120 volts, 50 Hz. The equivalent leakage impedance of the transformer referred to the 120 volt winding, denoted winding 2, is $Z_{eq2} = 0.0525 \angle 78.13^\circ \Omega$. Using the transformer ratings as base values, determine the per-unit leakage impedance referred to winding 2 and referred to winding 1. | 5 |
| Q. [5] Figure A shows the one-line diagram of a simple three-bus power system with generation at buses 1 and 3. The voltage at bus 1 is $V_1 = 1.025 \angle 0^\circ$. Voltage magnitude at bus 3 is fixed at 1.03 p.u. with a real power generation of 300 MW. A load consisting of 400 MW and 200 MVAR is taken from bus 2. Line impedances are marked in per unit on a 100 MVA base and line charging susceptances are neglected. Obtain the power flow solution by the Gauss-Seidel method up-to the first iteration only. Determine the line flows and line losses. Construct a power flow diagram showing the direction of line flow. | 10 |

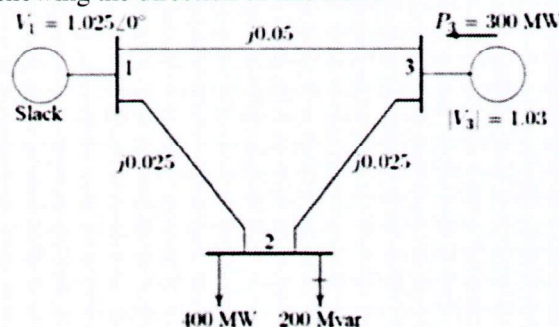


Figure: A

- | | |
|---|---|
| Q. [6] Make the Jacobian matrix for network shown in figure A. What will be the matrix size of Jacobian and their sub-matrix J_1 , J_2 , J_3 and J_4 ? Also, write the step-wise solution procedure of power flow using Newton-Raphson method for figure A. | 4 |
|---|---|