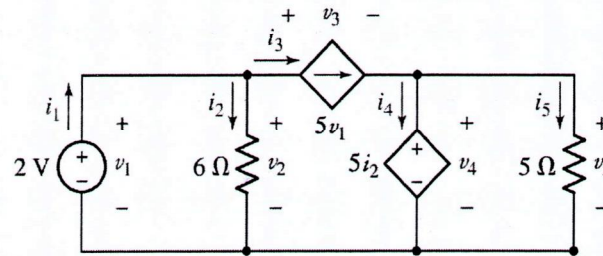


Branch : ECE / EEE

Title of the Course : Network analysis and synthesis

Maximum Marks: 25

1. (a) Determine a numerical value for each current and voltage (i_1 , v_1 , etc.) in the circuit of Fig. 1 4+2
(b) Calculate the power absorbed by each element and verify that they sum to zero.



2. Explain Thevenin's theorem with suitable example.

Explain Maximum power transfer theorem with suitable example.

3. (a) Find the value of v_p for the circuit as shown in fig 2 using superposition theorem. Also find the power consumed by 50 ohm resistor.

4. Determine $v_c(t)$ and $v_o(t)$ as labeled in the circuit represented in Fig. 3 for t equal to
 (a) 0^- (b) 0^+ (c) 10 ms (d) 12 ms.

4

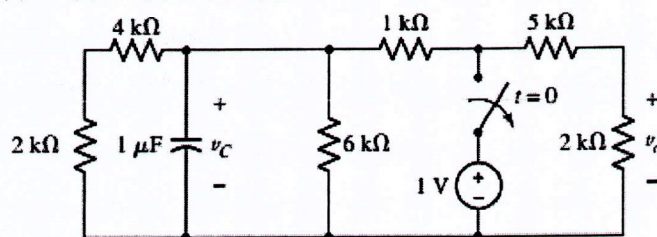


Fig 3

5. Refer to the network in Fig. 4. Find the following transfer functions:

5

- (a) $V_o(s)/V_s(s)$
- (b) $V_o(s)/I_s(s)$
- (c) $I_o(s)/I_s(s)$
- (d) $I_o(s)/V_s(s)$

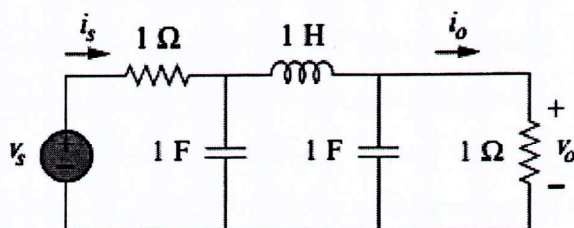


Fig 4