

Roll No.:.....

# National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : 5

Title of the Course : Power System Analysis

Course Code : EEL 302

Time: 3 hrs

Maximum Marks: 50

## Section A

Attempt all question

(10×1 = 10)

- Q. [1] What is single line diagram?
- Q. [2] For a given base voltage and base volt amperes, the per unit impedance value of an element is  $x$ . Calculate the per unit impedance value of this element when the voltage and volt amperes bases are both doubled.
- Q. [3] How the base values are chosen in per unit representation of a power system?
- Q. [4] Why is one of the buses taken as slack bus in a power system?
- Q. [5] What is the need for short circuit studies?
- Q. [6] Distinguish between symmetrical and unsymmetrical faults with neat sketch.
- Q. [7] Write the symmetrical components of a three phase system?
- Q. [8] What is sequence operator?
- Q. [9] Define swing curve. What is the use of this curve?
- Q. [10] Define transient stability of a power system

## Section B

Attempt any four

(4×5 = 20)

- Q. [1] What do you understand by percentage reactance? Why do we prefer to express the reactances of various elements in percentage values for short-circuit calculations?
- Q. [2] Derive an expression for fault current for double line-to-ground fault by symmetrical components method.
- Q. [3] Explain the step by step procedure of load flow solution for the Newton- Raphson method.
- Q. [4] Three zones of a single phase circuit are identified in the following Fig. A. The zones are connected by transformer  $T_1$  and  $T_2$ , whose rating are also shown. Given  $V_s = 220\angle 0^\circ$ ,  $X_{line} = 2\Omega$  and  $Z_{load} = (0.9 + j0.2)$ . Using base values of 30 kVA and 240 volts in zone 1, draw the per-unit impedance circuit and the per unit source voltage. Also calculate the load current both in per-unit and in amperes. Transformer winding resistances and shunt admittance branches are neglected.

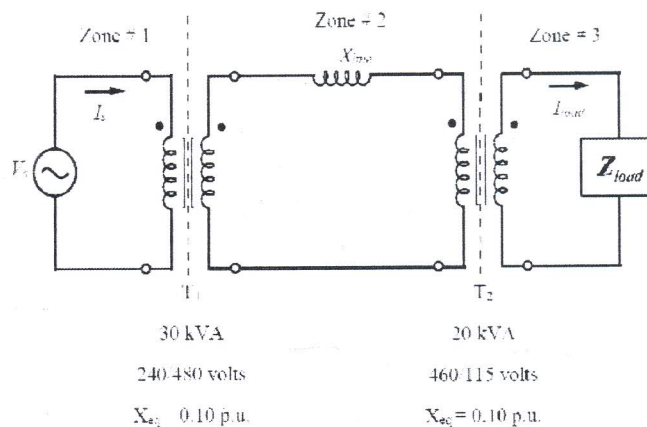


Fig. A

- Q. [5] Consider the impedance diagram of Fig. B in which the system parameters are given in per unit by  $Z_{11} = Z_{22} = j0.25$ ,  $Z_{12} = j0.2$ ,  $Z_{13} = j0.25$ ,  $Z_{23} = Z_{34} = j0.4$  and  $Z_{24} = j0.5$ . Evaluate the Y-bus matrix form give line specification.

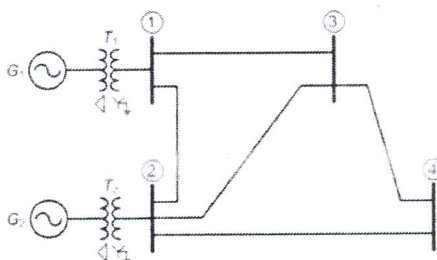


Fig. B

### Section C

Attempt any two

(2×10 = 20)

- Q. [1] A 3-phase transmission line operating at 10 kV and having a resistance of 1ohm and reactance of 4 ohm is connected to the generating bus-bars through 5 MVA step-up transformer having a reactance of 5%. The bus-bars are supplied by a 10 MVA alternator having 10% reactance. Calculate the short-circuit current, if it occurs, (i) at the load end of transmission line, (ii) at the high voltage terminals of the transformer in fig. C.

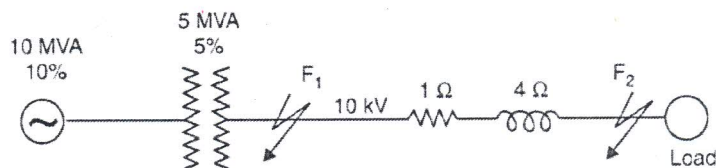


Fig. C

- Q. [2] Derive and explain the equal area criterion for stability of a power system.
- Q. [3] Derive swing equation and discuss the importance of stability studies in power system planning and operation.
- Q. [4] Derive the expression for the three phase power in terms of symmetrical components.