

Roll No.:

National Institute of Technology, Delhi

Mid Semester Examination, March 2022

Branch : ECE

Semester : VI

Title of the Course : Basics of VLSI

Course Code : ECB 351

Time : 1.5 Hours

Maximum Marks : 25


- All questions are compulsory.

[1] Draw circuit diagram to implement the following function. Also draw its layout using colour coding.

$$Y = [A.B + C.D]'$$

{3}

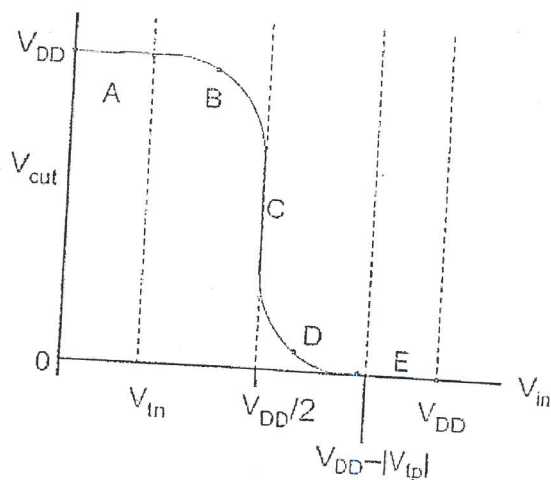[2] In the given voltage transfer characteristics of CMOS inverter write the mode of operation of NMOS and PMOS transistor in region A and region D (Show calculations)



{3}

[3] Define process transconductance parameter for MOSFET. How it affect the voltage transfer characteristics of CMOS inverter.

{3}

[4] Write short note on (i) Short channel effect and (ii) Body Effect

{3}

[5] What is Sclaing of MOS devices. Also explain the need of scaling.

{3}

[6] Consider a process technology for which $L_{min} = 0.4 \mu m$, $t_{ox} = 8 \text{ nm}$, $\mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}$ and $V_t = 0.7 \text{ V}$.

(a) Calculate oxide capacitance C_{ox} and K_n .

(b) For a MOSFET with $W/L = 8 \mu m / 0.8 \mu m$, calculate the values of V_{GS} and V_{DSmin} needed to operate the in the saturation region with a dc current $I_D = 100 \mu A$.

(c) For the device in (b), find the values of overdrive voltage V_{ov} and V_{GS} required to cause the device to operate as a $1000\text{-}\Omega$ resistor for very small V_{DS} . {5}

[7] A CMOS inverter with minimum sized transistors has $\beta_n = 0.2 \text{ mA/V}^2$, $\beta_p = 0.1 \text{ mA/V}^2$ and $V_{tn} = |V_{tp}| = 0.6 \text{ V}$. Assume $V_{DD} = 3.3 \text{ V}$.

a) What is the inverter gate switching threshold (midpoint) voltage?

b) What is the resistance for each transistors using general expression for MOSFET resistance in saturation? {5}