

**Aim ⇨** To design and obtain the frequency response of Second Order High Pass Filter [HPF].

**Equipment Required ⇨**

Resistors, Potentiometer, Capacitors, IC 741 OP-AMP, Function Generator, CRO, Breadboard & connecting wires.

**Theory ⇨**

A second-order high-pass filter allows signals with frequencies higher than a specified cut-off frequency  $f_L$  to pass while attenuating frequencies lower than  $f_L$ . The gain of the HPF at the cut-off frequency is reduced to 70.7% [or -3 dB] of its maximum value, indicating the transition between blocking and passing signals. Compared to first-order filters, second-order HPFs provide a steeper roll-off rate, allowing for better noise suppression and sharper cutoffs, making them ideal for applications requiring significant attenuation of low-frequency components.

**Roll-off Rate and Filter Order ↴**

A second-order HPF exhibits a roll-off rate of 40 dB/decade [or 12 dB/octave] below the cut-off frequency. This means that for every tenfold decrease in frequency, the gain decreases by 40 dB. Second-order filters achieve a sharper cutoff than first-order filters, which is beneficial in filtering out unwanted low-frequency noise and improving signal quality in various applications.

**Mathematical Expression ↴**

$$f_L = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}}$$

For simplicity, in a circuit where  $R_2 = R_3 = R$  and  $C_2 = C_3 = C$ , the cut-off frequency is given by:

$$f_L = \frac{1}{2\pi RC}$$

This formula, derived from filter design principles, indicates that the cut-off frequency is inversely proportional to the product of resistance and capacitance.

**Practical Considerations ↴**

The cut-off frequency, also known as the -3 dB frequency, is essential for determining the filter's effectiveness in separating desired high-frequency signals from unwanted low-frequency noise. In practical applications, second-order HPFs

are commonly used in audio processing, signal conditioning, and various electronic applications to enhance the quality of processed signals.

### Circuit Diagram ↗

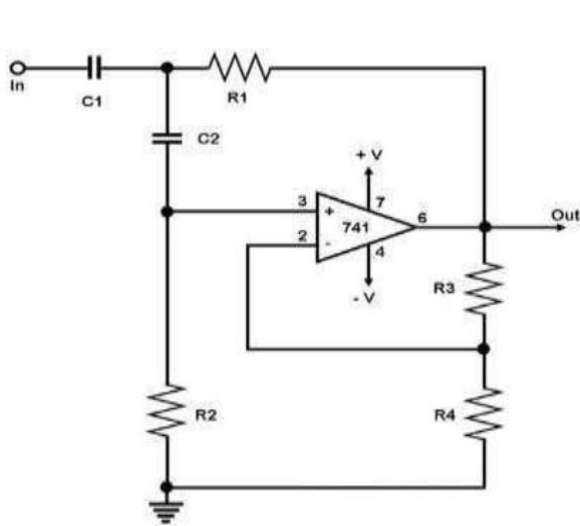


Fig. i) Second Order High Pass Filter

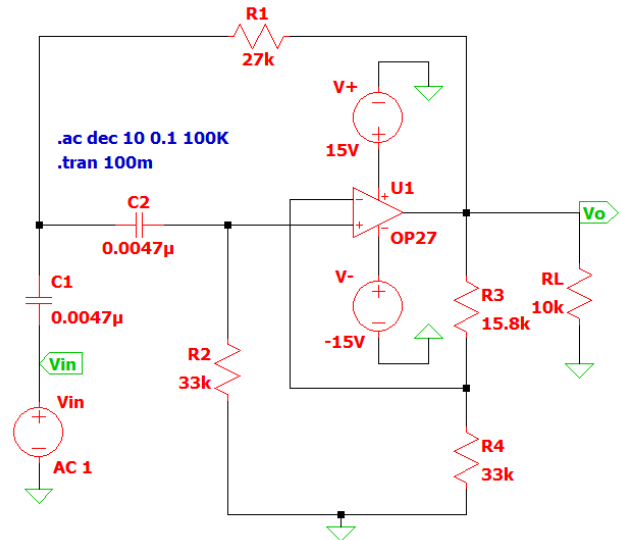


Fig. ii) LTSpice Implementation

### Observation Table ↗

#### ▪ Simulation Data ↗

S.No.	Input Freq f [Hz]	Gain Magnitude $\left  \frac{V_0}{V_i} \right $	Magnitude in dB $20 \log \left  \frac{V_0}{V_i} \right $
1	0.1	11.48n	-158.8
2	1	1.15μ	-118.8
3	10	114m	-78.8
4	100	11.48m	-38.8
5	1K	0.998	-0.009
6	10K	1.48	3.41
7	100K	1.48	3.40

## Graphs ⇌

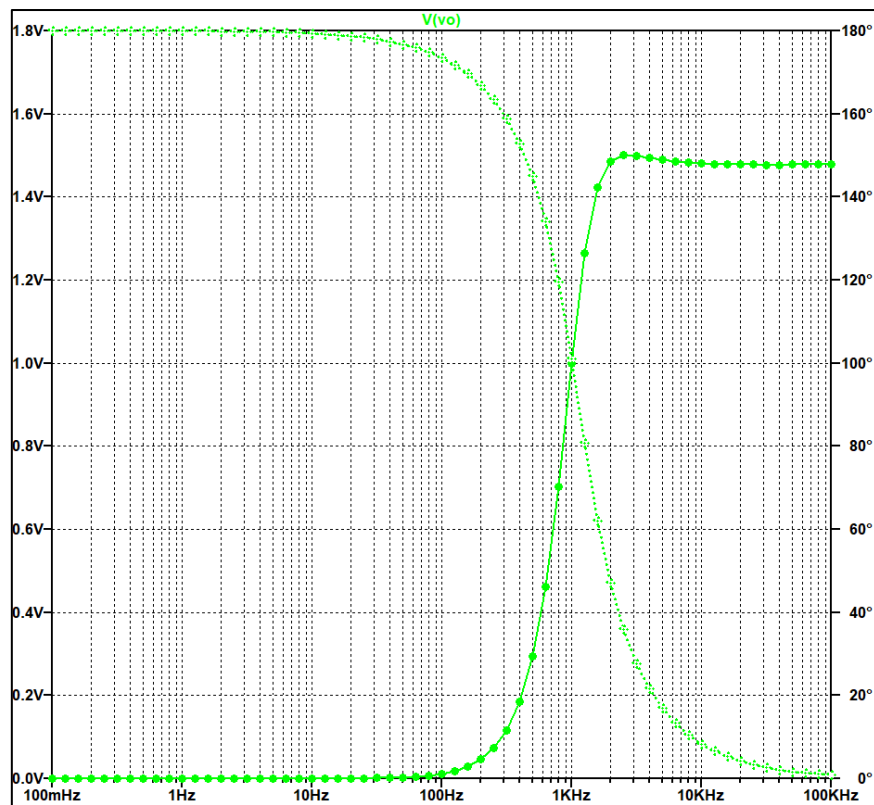


Fig. iii) Frequency Response [Linear]

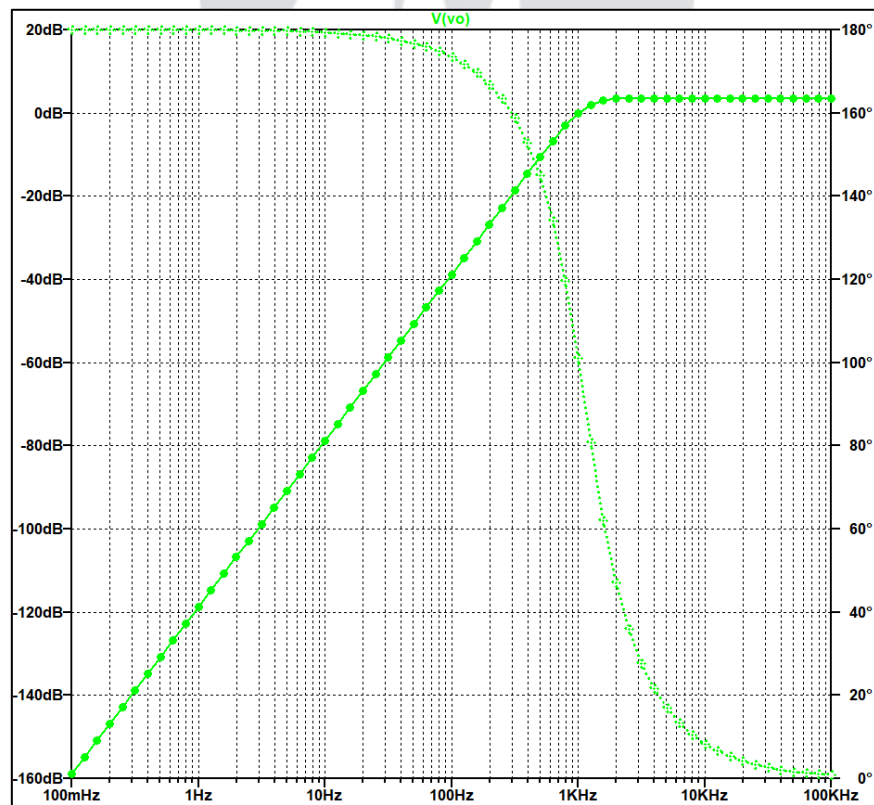


Fig. iv) Frequency Response [Decibel]

## Result ⇄

The experiment demonstrated the design and frequency response of a second-order high-pass filter. The filter successfully passed signals above the cut-off frequency  $f_L$  and attenuated lower frequencies at 40 dB/decade, confirming the expected behavior.

## Conclusion ⇄

The second-order high-pass filter was designed and tested successfully, aligning with the expected theoretical and simulation results. The filter exhibited the correct frequency response with the predicted roll-off rate below the cut-off frequency.

## Precautions ⇄

- Ensure all connections are correct and components are securely placed.
- Do not exceed the voltage ratings of components, especially the op-amp.
- Verify capacitor polarity and op-amp orientation.
- Double-check the circuit setup before powering on the equipment.

