

National Institute of Technology Delhi

B. Tech Examination March 2023

Branch	: Electrical Engineering	Semester	: IV
Title of the Course	: Power Systems	Course Code	: EEL 253
Maximum Marks	: 25	Time	: 1.5 Hours

Note : Attempt all questions. Symbols used in the questions are having their usual meaning. Assume if any data is missing.

Q.1 Attempt all questions.

- (a) Why the transmission lines 3 phase 3 wire circuits while distribution lines are 3 ϕ , 4 wire circuits? (1)
- (b) Write the primary distribution voltages in India. (1)
- (c) What is the difference between nominal T method and nominal π method? (1)
- (d) What are the factors to be considered while selecting a cable for a particular service? (1)
- (e) What is the use of power circle diagram? (1)

Q.2 Why the transmission voltages are in terms of kV? (2)

Q.3 An electric train runs between two two substations 6 km. apart maintained at voltages 600 V and 590 V respectively and draws a constant current of 300 A while in motion. The track resistance of go and return path is 0.04 ohm/km. Determine (4)

- a) the point of minimum potential along the track
- b) currents supplied by the two substations when the train is at the point of minimum potential

Q.4 Deduce an expression for inductance of 3-phase transposed unsymmetrically spaced transmission line. (4)

Q.5 Derive the expression for voltage regulation and transmission efficiency of short transmission line. (5)

Q.6 A balanced 3- ϕ load of 30 MW is supplied at 132 kV, 50 Hz and 0.85 p.f. lagging by means of a transmission line. The series impedance of a single conductor is $(20 + j52) \Omega$ and the total phase-neutral admittance is $315 \times 10^{-6} \text{ S}$. Using Nominal T method, determine (5)

- i) Characteristic Parameters ii) sending end voltage iii) regulation of the line
