

Roll No.:

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Mid-Semester Examination March, 2019

Branch : EEE

Semester : VIII

Title of the Course : HVDC & Flexible AC Transmission Systems

Course Code : EEL-451

Time: 2 Hours

Maximum Marks: 25

Note : All questions are compulsory

1. i) Give a comparison between HVDC system with EHVAC system based on economics, technical performance and reliability when bulk power is transmitted over a long distance. (2)
ii) Why the three-phase bridge circuit is invariably used for conversion and inversion in HVDC system? (1)
iii) Why commutation failure problem is frequency in inverter operation? Explain with the help of waveform. (2)
2. i) An HVDC bipolar link using a 6-pulse converter is supplying power of 500 MW at 100KV. The rectifier station is working at a delay angle $\alpha=15^\circ$. Estimate a) no load voltage b) AC voltage on the converter side of the transformer (2)
ii) A 3-phase fully controlled bridge converter is connected to a 400V, 50Hz supply having a source reactance of $0.3\Omega/\text{ph}$. The converter is operating at a firing angle of 70° . Determine the average load voltage and the overlap angle when the converter is supplying a steady current of 125A. (3)
3. a) Explain the terms:
i) Commutation group (1)
ii) pulse numbers applied to HVDC converters (1)
b) Sketch the voltage and current waveforms for Graet'z circuit (consider 2nd and 3rd valves are conducting and 4th valve is to be triggered) when
i) $\alpha=30^\circ, \mu=15^\circ$ ii) $\alpha=120^\circ, \mu=75^\circ$ iii) $\gamma=15^\circ$ (neglect overlap) (4)
4. Develop the equivalent circuit of a converter working as rectifier with an overlap angle μ and delay angle α for three/four valve conduction mode. Also, determine the equivalent resistance of the converter. (5)
5. Compare three phase one way rectifier with three-phase two way rectifier with respect to peak inverse voltage and volt ampere rating of transformer bank. Draw neat sketches and derive the expression used for both cases. (5)