

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Mid-Semester Examination September, 2019

Branch : Electronics & Communication
Engineering

Semester : Third

Title of the : Network Analysis and Synthesis
Course


Course Code : EEL 201

Time: 2 Hours

Maximum Marks: 25


ATTEMPT ALL THE QUESTIONS

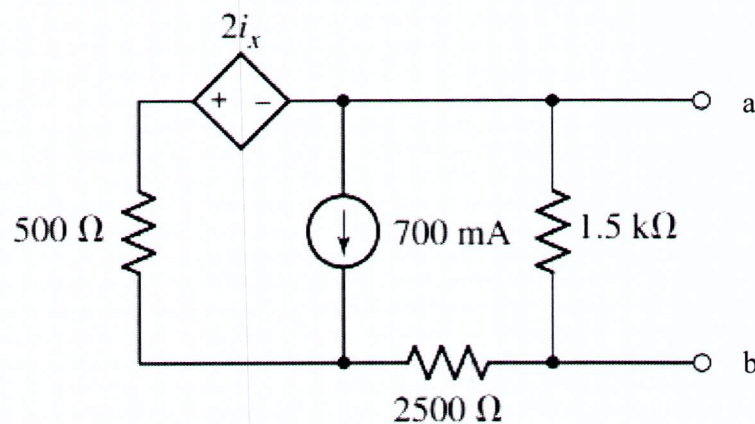1. Determine the Thevenin and Norton equivalent of the given circuit as seen by terminals a and b. (4)




2. (a) Determine the Thevenin equivalent connected to resistor R_L .

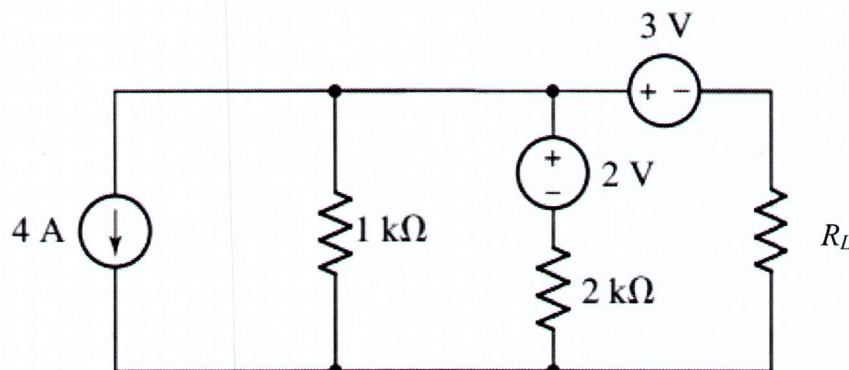
- (b) Select a value for R_L such that maximum power will be delivered to it and calculate the maximum power also. (4)



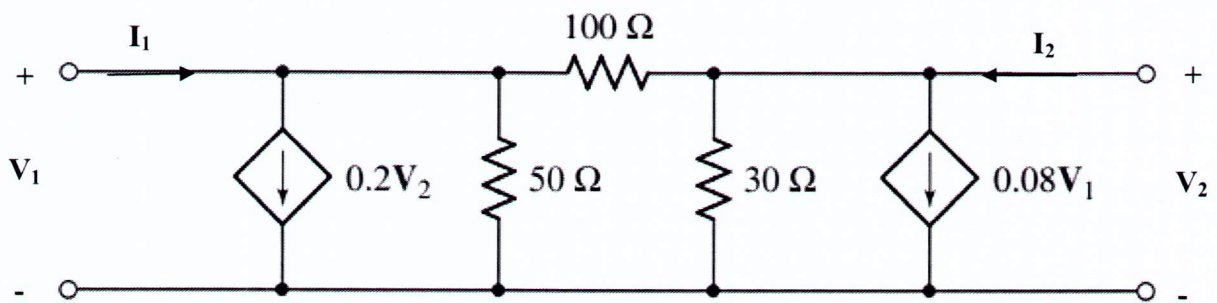
3. Obtain both the impedance and admittance parameters for the two-port network given below: (4)



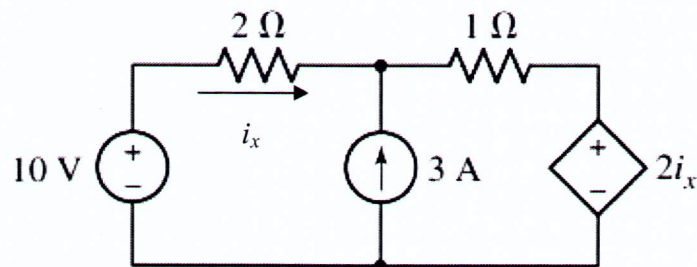
4. Using the superposition principle, determine the value of current i_x flowing through $2\ \Omega$ resistor. (3)



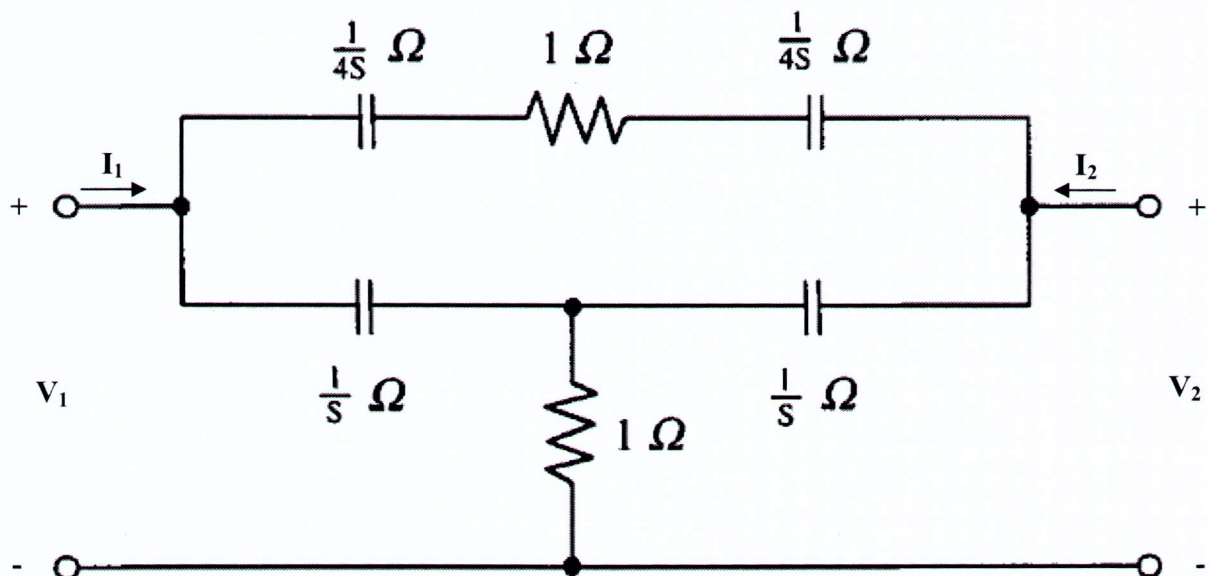
5. Determine the Y-parameters for the circuit shown below: (3)



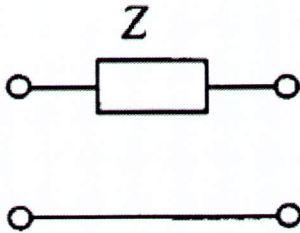
6. Find out the short circuit parameters for circuit (a), open circuit parameters for circuit (b) and hybrid parameters for circuit (c): (3)



(a)

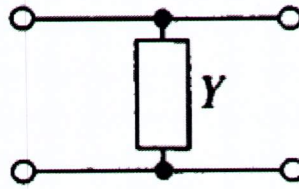


(b)

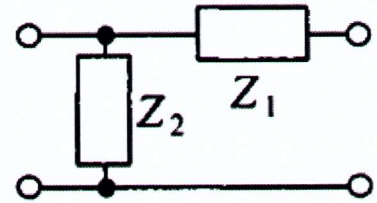


(c)

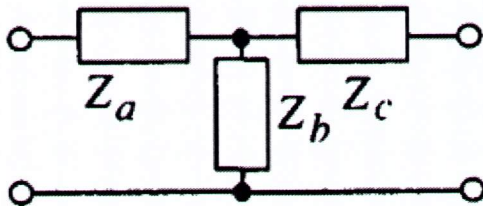7. Find out the hybrid and transmission parameters for each of the following circuits: (2)



(a)

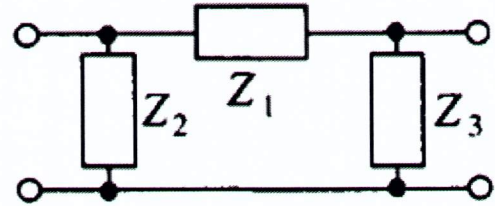

(b)

8. Find the voltage V_{ab} across the open circuit in the given circuit. (2)

