

# National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EE & ECE

Semester : 6<sup>th</sup>

Title of the Course : Power Electronics

Course Code : EEB 351

Time: 3 Hours

Maximum Marks: 50

Note : 1. Do not write anything on the question paper except Roll number

2. Assume any data suitably if found missing

3. Draw circuit diagram and waveforms neatly

---

**Section A: Answer all 10 questions. Each question carries 01 mark. [10×1=10]**

- Q1). What is the difference between MOSFET and BJT.
- Q2). Explain the significance of latching and holding current.
- Q3). Draw the circuit of 3 phase dual converter.
- Q4). Define commutation.
- Q5). What are merits and demerits of four quadrant choppers.
- Q6). Write applications of choppers.
- Q7). What is a feedback diode.
- Q8). What is a pulse width modulation? List the various PWM techniques.
- Q9). Define cycle selection.
- Q10). What is a cyclo-converter. What are its industrial applications?

**Section B. Each question carries 5 marks.**

**[4×5=20]**

- Q11). Draw the V-I characteristics of the SCR and explain its different modes. Explain  $di/dt$  and  $dv/dt$  ratings of SCR.
- Q12). Explain step up and step down chopper and derive the expression for their duty cycles. For a step down chopper, source voltage( $V_s$ )=230 V,  $R=10$  ohm calculate the average output voltage and rms output voltage if the drop across chopper is of 1 volt and duty cycle is of 0.4.
- Q13). Explain and draw the waveforms for a single phase inverter for RL load. Discuss the harmonic reduction technique by transformer connections.

**Q14).** Explain the two stage sequence control of voltage source controllers for RL load.

**Section C: Each question carries 10 marks.**

**[2×10=20]**

**Q15).** Explain the operation of 3 phase inverter employing 180 degree mode of operation. Draw the waveforms of phase voltages and line voltages, assume the star connected resistance load.

**Q16).** Explain the basic principle of a single phase to single phase step down cycloconverter for both continuous and discontinuous conduction modes and draw their waveforms for output voltage and output current.