

National Institute of Technology Delhi

Mid Semester Examinations-B. Tech

Branch- CSE and EEE

Course Name – Analog Electronics

Course Code - ECB-206

Year-2016, Semester-3rd

Maximum Marks – 25

Total Time: 2:00 Hours

All questions are compulsory.

Symbols have their usual meaning.

Assume any data, if it is missing.

Q.1-(a): How does the band theory differ from the free electron model in explaining the properties of metals? The resistivity of an intrinsic semiconductor is $4.5 \Omega \text{ m}$ at 20°C and $2.0 \Omega \text{ m}$ at 32°C . Find the energy gap in eV unit. (2.5)


(b): Why does the effective mass of the electron differ from its free mass toward an external force in the crystal lattice? Using the concept of de-Broglie wave show that effective mass of the electron in the crystal lattice is expressed by following relation: $m^* = \frac{\hbar^2}{d^2 E / dk^2}$. (2.5)

Or

What do you understand by thermal runaway? Derive the condition $V_{CE} < V_{CC}/2$ to avoid thermal runaway in transistor. (2.5+2.5)

 Q.2-(a): Consider a peak rectifier fed by a 60 Hz sinusoid having a peak $V_p = 100 \text{ V}$. Let the load resistance $R = 10 \text{ k}\Omega$. Find the value of the capacitance C that will result in a peak to peak ripple of 2 V. Also, calculate the fraction of the cycle during which the diode is conducting and the average and peak values of the diode current. (3)


(b): Determine C_1 and C_2 for the voltage doubling circuit as shown below to produce a 1% maximum output ripple. The input is a $\pm 12 \text{ V}$, 5 kHz square wave. (2)



Or

(b): For a BJT, the CB current gain $\alpha = 0.98$ and the collector-base junction reverse saturation current is $0.6 \mu\text{A}$. This BJT is connected in CE-mode and operated in active region with a base drive current of $20 \mu\text{A}$. Determine the collector current. (2)

 
Q.3: What are the characteristics of the ideal current and trans-conductance amplifiers? For the two port network as shown below determine: $\frac{V_o}{V_i}$, $\frac{I_o}{I_i}$, R_{in} and R_{out} . Further, comment that can this network be considered as an amplifier or not? (5)



Or

- (a) In the circuit shown, find the input impedance R_i in terms of the CE h parameters, R_L and R_E .
 (b) If $R_L = R_E = 1\text{ K}$ and assume the suitable h parameters, what is the value of R_i ?

(3+2)

 

Q.4: A CE amplifier employing an NPN transistor has load resistor R_C connected between collector and V_{CC} supply of +16V. For biasing, a resistor R_1 is connected between V_{CC} supply and base, resistor $R_2 = 30k\Omega$ is connected between base and ground and a resistor $R_E = 1\text{ k}\Omega$ is connected between emitter and ground. Draw the circuit diagram. Calculate the values of R_1 and R_C and the stability factor S , if $V_{BE} = 0.2\text{ V}$, $I_E = 2\text{ mA}$, $\alpha = 0.985$ and $V_{CE} = 6\text{ V}$. (5)

Q.5- Define the pinch-off voltage of the JFET. A JFET amplifier with stabilized biasing circuit shown below has following parameters: $V_P = -2\text{ V}$, $I_{DSS} = 5\text{ mA}$, $R_L = 910\ \Omega$, $R_F = 2.29\text{ k}\Omega$, $R_1 = 12\text{ M}\Omega$, $R_2 = 8.57\text{ M}\Omega$ and $V_{DD} = 24\text{ V}$. Determine the value of drain current I_D at the operating point. Also verify that FET will operate in pinch-off region. (5)

