

# National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE

Semester : 5<sup>th</sup>

Title of the Course : Power System Analysis

Course Code : EEL302

Time: 2 Hours

Maximum Marks: 25

**Note:** 1. Answer all the questions.

2. Do not write anything on the question paper except Roll number

3. Assume any data suitably if found missing

**Q.1.** Find the  $Y_{bus}$  for the following line data.

[5]

Line between Bus No.	Conductance	Susceptance	Shunt admittance
1-2	2	-j20	-
2-3	3.5	-j18	-j6
3-4	3	-j15	-
4-1	4.5	-j28	j5
1-3	6	-j30	-j8

Further modify the  $Y_{bus}$  if a line having admittance of  $(8-j15)$  is connected in between buses 2 to 4 with a transformer of turn ratio 1:50.

**Q.2** For a network, bus data is as follows at the base of 100MVA, 230kV.

[8]

Bus No	$P_G$	$Q_G$	$P_D$	$Q_D$	$ V (\text{pu})$
1	250	150	-	-	1
2	100	75	80	100	.95
3	125	60	100	105	.98
4	200	60	100	-	1.05

Line Data is as follows

Line between Bus No.	Conductance	Susceptance	Shunt admittance
1-2	2.5	-j21	-j6
1-3	3.8	-j22	-j6
2-4	4.2	-j15	-j6
3-4	4.5	-j28	-j6

Using fast decoupled method determine the first iteration solution to the power flow problem.

**Q.3** Compute all the generalized terms of J matrix for N-R load flow problem in polar form. [4]

**Q.4** Develop a node equation for a line of admittance  $Y_{jk}$  between buses  $j$  and  $k$  if a transformer of turns ratio 1:20 and a phase shifter  $1.5\angle 30^\circ$  connected in series between  $j$  and  $k$ . [4]

**Q.5** Determine the  $Z_{bus}$  for the network shown in Fig. 1. [4]

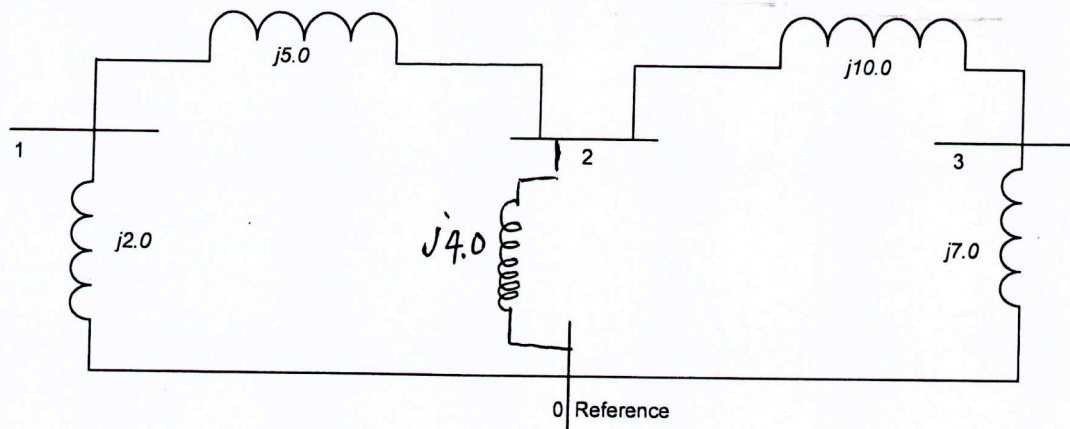


Fig.1