

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE and ECE.

Semester : 1st

Title of the Course : Introduction to Electrical &

Course Code : EEB100

Electronics Engineering

Time: 3 Hours

Maximum Marks: 50

Note : 1. Do not write anything on the question paper except Roll number

2. Assume any data suitably if found missing

Section A: Answer all 10 multiple choice questions. Each question carries 01 mark. [10×1=10]**A1.** A charge of 240 C is transferred in 2 min, the current flowing is?

- (a)
- 120 A
- (b)
- 480 A
- (c)
- 2 A
- (d)
- 8 A

A2. The peak factor of a sine waveform is

- (a)
- 1.11
- (b)
- 1.414
- (c)
- 2
- (d)
- 1.5

A3. The form factor of a half wave rectified sine wave is

- (a)
- 2
- (b)
- 1.11
- (c)
- 1.414
- (d)
- 1.57

A4. If the doping level of a crystal diode is increased, the breakdown voltage

- (a) Remains same (b) is decreased (c) is increased (d) none

A5. The number of depletion layers in a transistor is

- (a) three (b) two (c) one (d) four

A6. A transistor is a _____ operated device

- (a) current (b) voltage (c) both (d) none

A7. The equivalent resistance of the primary of a transformer having $K=5$ and $R_1=0.5\Omega$ when referred to secondary becomes _____ Ω

- (a)
- 0.5
- (b)
- 0.02
- (c)
- 0.004
- (d)
- 2.5

P.T.O

1 of 2

A8. The primary and secondary induced e.m.fs E_1 and E_2 in a two-winding transformer are always

- (a) equal in magnitude
- (b) anti-phase with each other
- (c) in-phase with each other
- (d) determined by load on transformer

A9. The 2's complement of 1000_2 is

- (a) 0111
- (b) 0101
- (c) 1000
- (d) 0001

A10. A flip flop which can have an uncertain output is:

- (a) J-K flip flop
- (b) S-R flip flop
- (c) D flip flop
- (d) T flip flop

Section B: Answer any 4 questions. Each question carries 5 marks.

[4×5=20]

B1. A 20 kHz clock signal is applied to a J-K flip flop with $J = K = 1$. Sketch the output waveform and determine its frequency.

B2. Use the 1's and 2's complements for the following binary subtractions

- (i) 1111-1011
- (ii) 110011-100101
- (iii) 100011-111010
- (iv) 1101-1011
- (v) 1000-11

B3. Explain how zenor diode can be used in voltage regulator with neat diagram.

B4. Derive the emf equation of transformer.

B5. Explain the working of simple a.c generator.

Section C: Answer any 2 questions. Each question carries 10 marks.

[2×10=20]

C1. A 230 / 460 V transformer has a primary resistance of 0.2Ω and a reactance of 0.5Ω and the corresponding values for the secondary are 0.75Ω and 1.8Ω respectively. Find the secondary terminal voltage when supplying (a) 10 A at 0.8 p.f lagging, (b) 10 A at 0.8 p.f leading.

C2. Three inductive coils, each with a resistance of 15Ω and an inductance of $0.03 H$ are connected (i) in star and (ii) in delta, to a 3-phase, 400V, 50 Hz supply. Calculate for each of the above case (a) phase current and line current, (b) total power absorbed.

C3. Explain the characteristics of different types of DC generators.