

Roll No .....

# National Institute of Technology, Delhi

Name of the Examination: B.Tech.

Re-Mid Semester Examination (October, 2023)

Branch : ECE & EE

Semester : 5th

Title of the Course : IC Applications

Course Code : ECBB 304

Time: 1 Hour 30 Minutes

Maximum Marks: 25

Note: All questions are compulsory.

COURSE OUTCOMES		COGNITIVE LEVELS
C01	Study of basics of operational amplifier ideal and practical	Understanding (Level II)
C02	Application of operational amplifier	Analyzing (Level IV)
C03	Study and analysis of opamp filters	Evaluating (Level V)
C04	Comparator, convertor circuit analysis	Analyzing (Level IV)

Course Outcomes(CO's)	C01	C02
Questions No.	Q1, Q2	Q3, Q4, Q5

Answer the following questions. All questions carry equal marks.

- 1) Find the expression of voltage gain for inverting opamp configuration with negative feedback.
- 2) Define input bias current and derive its mathematical expression.
- 3) Why gain falls for specific frequency ranges? Find the expression for gain magnitude and phase angle for open loop opamp configuration.
- 4) What is the power absorbed by the 4-k $\Omega$  resistor below?

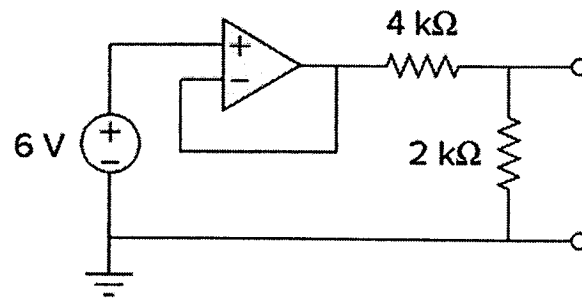


Figure 1

5. Find output offset voltage. Following values are given:

$$R_f = 2K$$

$$R_{in} = 150K$$

$$\text{Input offset} = 1.2 \text{ mV}$$

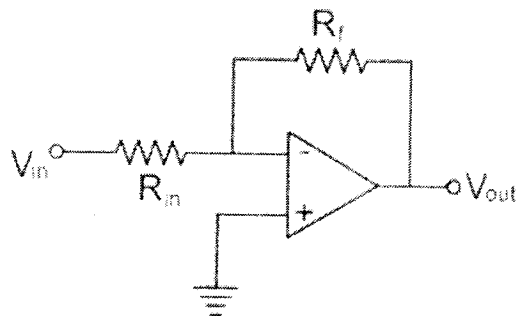


Figure 2