

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : ECE

Semester : III

Title of the Course : Digital Electronics

Course Code : ECB 202

Time: 2 Hours

Maximum Marks: 25

Note:

- All Questions are compulsory.

-
- | | |
|--|---|
| Q1. Design a 1-bit comparator circuit using universal logic gates. | 3 |
| Q2. Implement the following function using a 4 to 16 line decoder. $F(a, b, c, d) = a\bar{b} + acd + d + b\bar{c}$ | 3 |
| Q3. Implement a full adder circuit using 2 half adders and basic logic gates. | 3 |
| Q4. Find the minimal SOP and POS (both) for the following functions: $f(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10, 14, 15). d(0, 7, 12)$ | 3 |
| Q5. Explain the function of parity generator and design an even parity generator circuit. | 3 |
| Q6. Design a logic circuit that accepts a 3 bit binary number and generates an output binary number equal to the square of the input number. | 5 |
| Q7. Draw the circuit of 4 bit BCD adder and explain its function with the help of 4-bit BCD number addition example. | 5 |

***** END OF THE QUESTION PAPER *****