

Roll No.:.....

National Institute of Technology, Delhi

Name of the Examination: B. Tech (Make Up)

Branch

: ECE

Semester

: IV

Title of the Course

: ANALOG ELECTRONICS

Course Code

: ECB 252

Time: 3 Hours

Maximum Marks: 50

- Answers should be CLEAR AND TO THE POINT. All parts of a single question must be answered together. ELSE QUESTION SHALL NOT BE EVALUATED.

- A p-n-p Ge transistor is used in the self-biasing arrangement given in figure 1, where $V_{cc} = 4.5$ V, $R_c = 1.5$ K Ω , $R_e = 0.27$ K Ω , $R_2 = 2.7$ K Ω , $R_1 = 27$ K Ω and $|V_{BE}| = 0.2$ V. If $\beta = 44$, find: [1+2+2]
(a) The stability factor, S (b) the Q-point, (c) recalculate these values (S and Q-pt) if the base spreading resistance of 690 Ω is taken into consideration.
- In the Darlington stage, shown in figure 2, $V_{cc} = 24$ V, $\beta_1 = 24$, $\beta_2 = 39$, $V_{BE} = 0.6$ V, $R_c = 330$ Ω and $R_e = 120$ Ω . If at the Q-point of second transistor, $V_{CE2} = 6$ V, determine [5]
(a) resistance value, R, (b) stability factor 'S' defined as $S = dI_C / dI_{CO1}$.
- Consider second collector to first emitter feedback pair configuration in figure 3. Calculate (a) A_{v1} (b) A_{v2} (c) A_v (d) β (e) A_{vf} (f) R_o (g) R_{of} and (h) R_{if} for the amplifier configuration. Assume, $R_s = 0$, $h_{fe} = 50$, $h_{ie} = 1.1$ K, $h_{re} = h_{oe} = 0$ and all transistors are identical. [8x2]
- The transistor in following figure 4, is connected as CE amplifier and the h-parameters are given in the following table. If $R_s = R_L = 1$ K Ω , find (a) A_v (b) A_{vs} (c) A_i and (d) A_{is} . [4]

Parameters	Values
$h_{11} = h_i$	1100 Ω
$h_{12} = h_r$	2.5×10^{-4}
$h_{21} = h_f$	50
$h_{22} = h_o$	25 μ A/V
$1/h_o$	40 K

- Show that the overall h parameters of the accompanying two-stage cascaded amplifier, shown in figure 5, are: [5]

$$(a) h_{11} = h_{11}' - \frac{h_{12}' h_{21}'}{1 + h_{22}' h_{11}''} h_{11}''$$

$$(b) h_{12} = \frac{h_{12}' h_{12}''}{1 + h_{22}' h_{11}''}$$

$$(c) h_{21} = \frac{h_{21}' h_{21}''}{1 + h_{22}' h_{11}''}$$

$$(d) h_{22} = h_{22}'' - \frac{h_{12}'' h_{21}''}{1 + h_{22}' h_{11}''} h_{22}'$$

- Write true (T)/ false (F) against each statement. [10x0.5]

- Compensation circuits refer to resistive biasing circuits.
- Negative feedback is more suitable for amplification.

- (c) Tentatively Q-point for a self-bias circuit will be at the middle of load line.
- (d) Q-point should be fixed with $V_{CEQ} < V_{CC}/2$ in order to avoid thermal runaway.
- (e) The term low frequency implies the range of frequencies of the input signal in which effects of internal capacitances are considered.
- (f) CC amplifier provides current gain instead of voltage gain.
- (g) A CE transistor stage connected in series with a CB transistor stage provides the cascode combination.
- (h) Difference amplifier is used to amplify the difference between two signals.
- (i) At α -cut off frequency, the high frequency α falls to $0.707 \alpha_0$.
- (j) At high frequency operation, h-parameters are real numbers.

7. Write brief notes on followings:

[2+2]

- (a) CB physical model of transistor with early feedback generator and base spreading resistance.
- (b) Transistor two port device and hybrid model.

8. Opt for the correct option only.

[6x1]

- (a) In a self-bias circuit, the stability increases, as the base resistance **increases/decreases/ remains constant**.
- (b) An amplifier supplies output current proportional to the signal voltage and independent of R_s and R_L known as- **trans-resistance/ trans-conductance/ current** amplifier.
- (c) Physical model of transistor includes **early feedback generator/base spreading resistance /both**.
- (d) Operation of feedback network is **unidirectional/bi-directional/omni-directional**.
- (e) For an oscillator, the source of electrical input is **D.C. supply/ac source/generated noise**.
- (f) From a circuit design point of view, more practical parameter to measure **transistor gain/transistor gain with feedback/transistor gain with feedback and including source**.