

Roll No.: .....

# National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : 5

Title of the Course : Power System Analysis

Course Code : EEL 302

Time: 2hr

Maximum Marks: 25

Note: Attempt all questions.

- |   | Mark |
|---|------|
| Q. [1] How the base values are chosen in per unit representation of a power system?   | 2    |
| Q. [2] Why one of the buses taken as slack bus in a power system?   | 2    |
| Q. [3] If the reactance in ohms is 15 ohms, find the p. u. value for a base of 15 KVA and 10 KV.  | 2    |
| Q. [4] What are the different types of buses in power systems? What are the quantities specified at each bus?   | 3    |
| Q. [5] Consider the impedance diagram of Fig. A in which the system parameters are given in per unit by $Z_{11} = Z_{22} = j0.25$ , $Z_{12} = j0.2$ , $Z_{13} = j0.25$ , $Z_{23} = Z_{34} = j0.4$ and $Z_{24} = j0.5$ . Evaluate the Y-bus matrix from give line specification. | 6    |

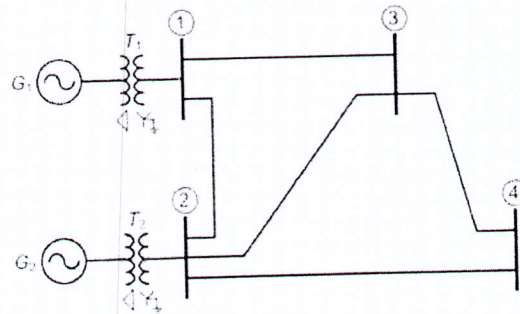


Fig. A

- Q. [6] A single-phase two winding transformer is rated 20 kVA, 480/120 volts, 50 Hz. The equivalent leakage impedance of the transformer referred to the 120 volt winding, denoted winding 2, is  $Z_{eq2} = 0.0525 \angle 78.13^\circ \Omega$ . Using the transformer ratings as base values, determine the per-unit leakage impedance referred to winding 2 and referred to winding 1. 10