

National Institute of Technology, Delhi

B. Tech. Examination

Make up Examination May, 2019

Branch	: Electrical & Electronics Engineering	Semester	: Fourth
Title of the Course	: Introduction to Electrical and Electronics Engineering	Course Code	: EEB 100

Time: 3 Hours

Maximum Marks 50

Note : Symbols used in the questions are having their usual meaning. Assume if any data is missing.

Section- A- Attempt all questions. Write the short answer.

(1x10)

Q.1 The open collector outputs of two inputs NAND gates are connected to a common pull up resistor is the input to the gates are P,Q and R, S respectively, The output is equal is

- (a) $\overline{PQ} \cdot \overline{RS}$ (b) $\overline{PQ} + \overline{RS}$ (c) $PQ + RS$ (d) $PQRS$

Q.2 The superposition theorem is essentially based on the concept of

- (a) duality (b) reciprocity (c) linearity (d) nonlinearity

Q. 3 single phase diode bridge circuit is supplied from a 100 V, 50Hz ac source to feed a dc load at an average current of 50A. The reduction in voltage due to a source inductance of 0.15 mH and internal drop at diode having the forward volt-drop relation of $(0.5 + 0.02i)$ volts is:

- a) 1% b) 2% c) 5% d) 3%

Q. 4 A NPN Si transistor is meant for low current audio amplification. Match its following characteristics against their values :

Characteristics	Values
(A) V_{EB} max	(P) 0.7 V
(B) V_{CB} max	(Q) 0.2 V
(C) V_{CE} max	(R) 6 V
	(S) 50 V

(a) $A \rightarrow P, B \rightarrow R, C \rightarrow S$


(b) $A \rightarrow R, B \rightarrow P, C \rightarrow S$

(c) $A \rightarrow S, B \rightarrow R, C \rightarrow P$

(d) $A \rightarrow P, B \rightarrow R, C \rightarrow Q$

Q. 5 The Gray code for decimal number 6 is equivalent to-----

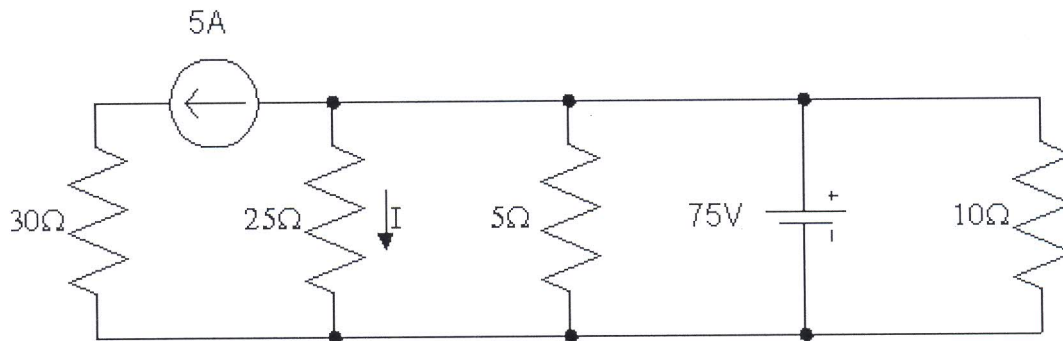Q.6 In a below given electric circuit find the value of 'I'




Q. 7 Why is Transformer Rated in KVA, not in KW ?

Q.8 The minimum number of resistor require to form a series –parallel combination is.....

Q.9 When a capacitor in a circuit is fully charged, it behaves as a short circuit (True/False)

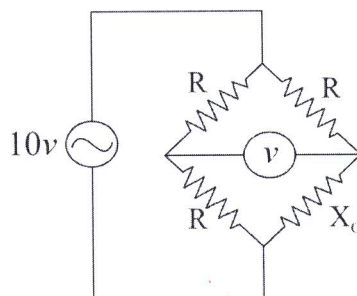
Q.10 In the bridge circuit shown in fig. when $\frac{X_c}{R} = 1$ the voltmeter reads;



Section- B- (Attempt any four questions)

(5x4)

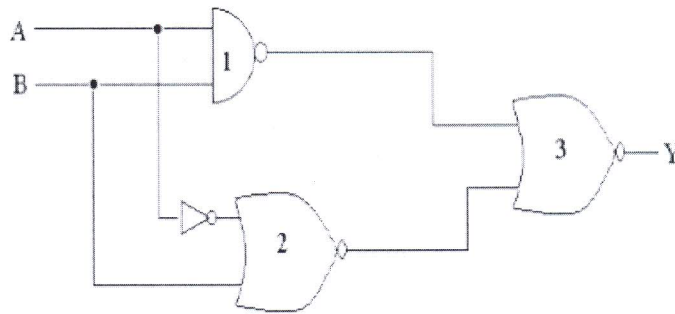
Q. 11 Find the Boolean expression for the logic circuit shown below:



Q. 12 With the help of neat diagram and expression derive the verification of maximum power transfer theorem.

Q. 13 A string of Deepawali lights consists of forty 3-W, 6-V bulbs connected in series. Calculate the current flows when the string is plugged into a 240-V socket, and what is the net hot resistance of each bulb.

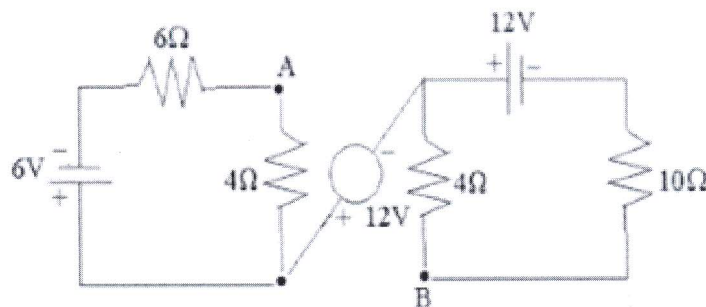Q.14 Obtain the voltage V_{AB} across terminals A and B in the network, shown in figure



Q.15 One meter long metallic wire is broken into two unequal parts P & Q. Part P of the wire is uniformly extended into another wire R. Length of R is twice the length of P and resistance of R is equal to that of Q. Find a) The ratio of the resistances of P and R, and b) The ratio of the length of P and Q.


Section- C- (Attempt any two questions)

(10x2)

Q. 16 For a 1- ϕ . 50-Hz. 150-kVA transformer, the required no-load voltage ratio is 5000-V/250-V. Find

- The number of turns in each winding for a maximum core flux of 0.06 Wb,
- The efficiency at half rated kVA, and unity power factor
- The efficiency at full load, and 0.8 power factor lagging, and
- The kVA load for maximum efficiency, if the full-load copper losses are 1800W and core losses are 1500W.

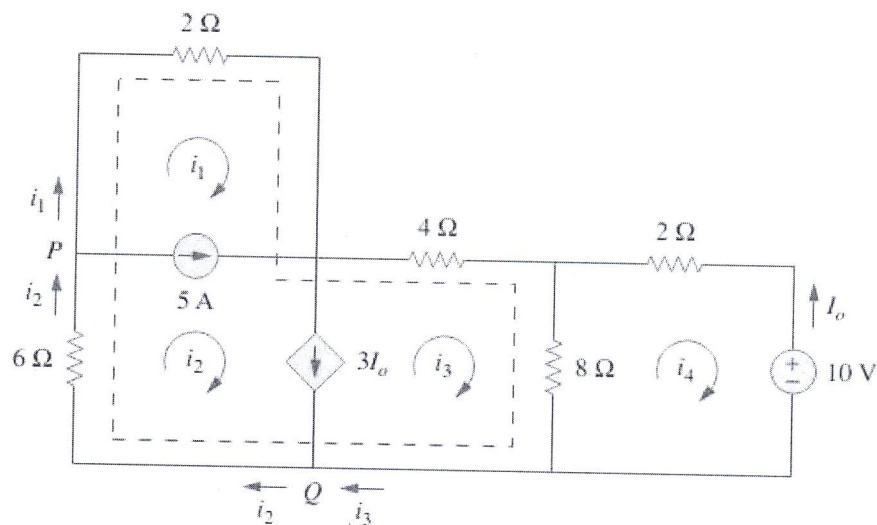Q. 17 Find i_1 and i_4 in the following circuit using mesh analysis:



Q.18 The transistor circuit shown uses a silicon transistor with $V_{BE} = 0.7V$, $I_C \approx I_E$ and a dc current gain of 100. The value of V_0 is:

