

*National Institute of Technology, Delhi*

Name of the Examination: B. Tech

Branch : ECE

Semester : IV

Title of the Course : Analog Electronics

Course Code : ECB 252

Time: 2 Hours

Maximum Marks: 25

- Questions are printed on BOTH sides. Answers should be CLEAR AND TO THE POINT.
- All parts of a single question must be answered together. ELSE QUESTION SHALL NOT BE EVALUATED.

1. For the circuit in figure 1, derive the expression for stability factor  $S$ , in terms of  $\beta$ .  $V_{BE}$  can be neglected. [3]
2. In the circuit shown in figure 2,  $V_{CC} = 24\text{ V}$ ,  $R_c = 10\text{ K}\Omega$ , and  $R_e = 270\Omega$ . If a Si transistor is used with  $\beta = 45$ , and if under quiescent conditions  $V_{CE} = 5\text{ V}$ , then determine (a) value of  $R$  and (b) stability factor ( $S$ ). [4]
3. Determine the minimum value of current gain ( $\beta$ ) for the transistor in figure 3, required to drive in saturation when  $V_{in} = +5\text{ V}$ ,  $V_{BE(sat)} = 0.8\text{ V}$  and  $V_{CE(sat)} = 0.12\text{ V}$ . [3]
4. A Si transistor with  $V_{CE(sat)} = 0.2\text{ V}$ ,  $h_{FE} = 100$ ,  $V_{BE(sat)} = 0.8\text{ V}$  is used in the circuit in figure 4. [3]
  - (a) Find the minimum value of  $R_L$  for which the transistor is in saturation. Assume,  $I_C \sim I_E$ ,  $V_{BB} = 12\text{ V}$  and  $V_{CE} = 10\text{ V}$ .
  - (b) Determine the output ( $V_0$ ) at saturation for  $R_L = R_{L, \min}$  for which transistor remains in saturation.
5. If the Si transistor used in the circuit in figure 5 has a minimum value of  $\beta = h_{FE} = 30$ , determine whether the transistor is in cut off or active or in saturation region?  $V_1 = +12\text{ V}$ ,  $V_2 = -12\text{ V}$ ,  $R_1 = 15\text{ K}\Omega$ ,  $R_2 = 100\text{ K}\Omega$ ,  $R_c = 2.2\text{ K}\Omega$ . Also find the output ( $V_0$ ). [5]
6. For the self-bias circuit in figure 6, the Q-pt is assumed to be exactly at the middle of the dc-load line. [2]
 

What will be the expression for the total combination of  $R_c$  and  $R_e$ , in terms of  $V_{CC}$  and power dissipation ( $P_{DQ}$ ) at Q-pt.
7. Answer the followings only writing either True (T) or False (F) against each one. [5]
  - (a) In a self-bias circuit, the stability increases as the base resistance increases.
  - (b) For  $R_b = 0$  and  $R_e$  not equal to 0, transistor can not be operated in active region.
  - (c) Rate of change of stored charge is responsible for storage time in switching.
  - (d) Heavily doped base in HBT, increases the base resistance.
  - (e) Stabilization techniques of bias stability uses thermistors.

 


Figure 1.

 


Figure 2.

 


Figure 3

 


Figure 4

 


Figure 5

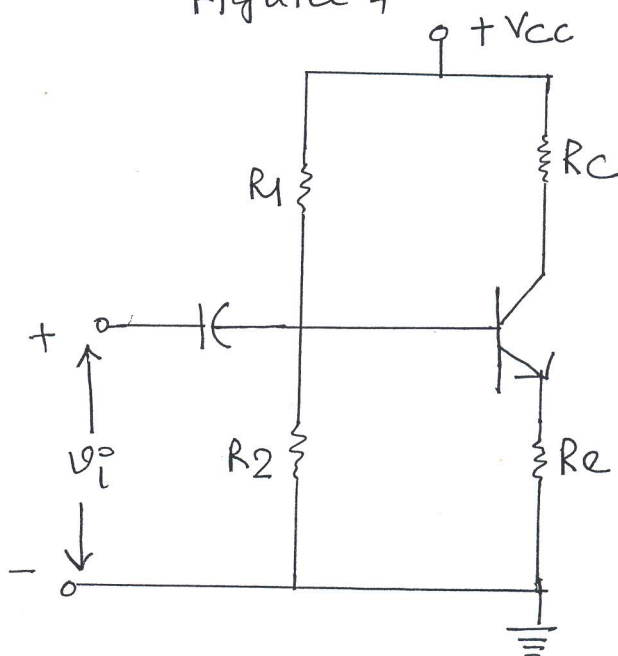


Figure 6