

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE and ECE.

Semester : 1st

Title of the Course : Introduction to Electrical &
Electronics Engineering

Course Code : EEB100

Time: 2 Hours

Maximum Marks: 25

- Note : 1. This paper contains 6 questions in 2 printed pages.
2. Answer all the questions.
3. Do not write anything on the question paper except Roll number

1. Evaluate R_{AB} of the network shown in Fig.1.

[4]

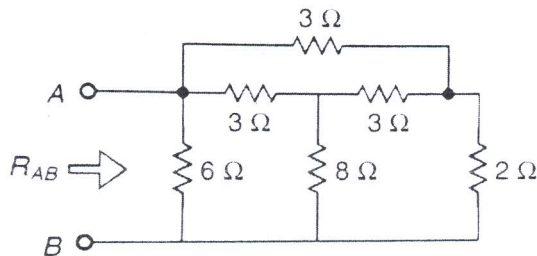


Fig. 1

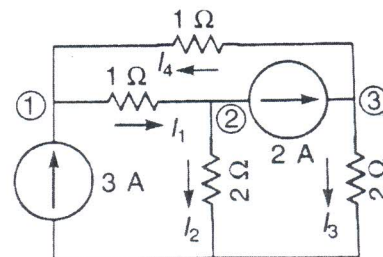


Fig. 2

2. Find different branch currents in the circuit shown in Fig. 2 using nodal analysis [4]
3. Determine the current through $R_L = 2\Omega$ in the circuit of Fig. 3 using superposition theorem. [4]

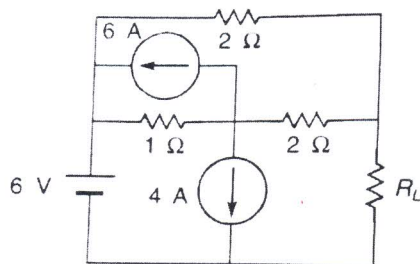


Fig. 3

4. A balanced three-phase system supplies an unbalanced delta connected load made up of two resistors of 100Ω , 200Ω and a coil having an inductance of $0.3H$ with negligible resistance. The line to line voltage is $100V$ and supply frequency is $50Hz$. Calculate (i) total power in the system, and (ii) the total reactive volt amperes.

[4]

5. The input power to a 1.6 kV , 50 Hz , three-phase motor is measured by using 2 wattmeter method. The motor is running on full-load and efficiency is 86% . The readings are 255 kW and 85 kW , respectively. Determine: (i) input power, (ii) power factor, (iii) line current, and (iv) output power. [4]
6. Explain the working of half wave rectifier and full wave bridge rectifier. [5]