

National Institute of Technology, Delhi


Name of the Examination: B. Tech.

Branch	: ECE	Semester	: VI th
Title of the Course	: Basic of VLSI	Course Code	: ECB 351
Time	: 3 Hours	Maximum Marks	: 50

Note: All questions are compulsory.

- Briefly explain the following with suitable diagrams 10
 - Channel length modulation
 - Short channel effects
 - Rise time, Fall time, Delay time
 - BiCMOS technology
 - 6T SRAM cell
- Calculate the threshold voltage V_{TO} at $V_{SB} = 0$, for a polysilicon gate n-channel MOS transistor, with the following parameters: substrate doping density $N_A = 4 \times 10^{18} \text{ cm}^{-3}$, polysilicon gate doping density $N_D = 2 \times 10^{20} \text{ cm}^{-3}$, gate oxide thickness $t_{ox} = 16 \text{ \AA}$, and oxide-interface fixed charge density $N_{ox} = 4 \times 10^{10} \text{ cm}^{-2}$. Assume $n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$ and Fermi potential of polysilicon gate is 0.55 V. 5
- Consider the circuit shown in figure 1 below. 6
 - Determine the logic function F.
 - Design a circuit to implement the same logic function by NOR gates in the transistor-level schematic using pseudo nMOS technology.
 - Design a circuit to implement the same logic function, in the transistor-level schematic using CMOS technology.

Figure 1

 

- Consider a CMOS inverter circuit with the following parameters: 6
 $V_{DD} = 3.3 \text{ V}$, $V_{TO,n} = 0.6 \text{ V}$, $V_{TO,p} = -0.7 \text{ V}$, $k_n = 200 \mu\text{A/V}^2$, $k_p = 80 \mu\text{A/V}^2$. Calculate the noise margins of the circuit. Notice that the CMOS inverter being considered here has $k_R = 2.5$ and $V_{TO,n} \neq |V_{TO,p}|$ hence, it is not a symmetric inverter.
- Explain CMOS Transmission gates. Determine the equivalent resistance in different regions of operations. 6

6. Consider the domino CMOS circuit shown in figure 2 below. Using the input voltage waveforms illustrated in figure 3, determine the output voltage waveform. 4

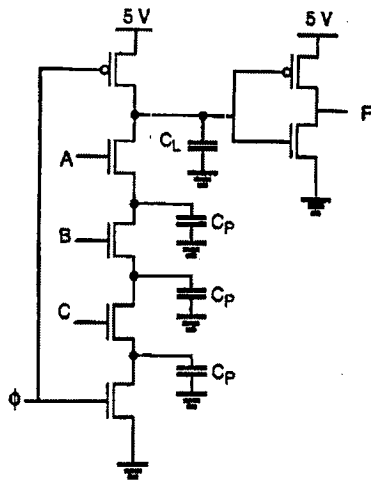


Figure 2


 


Figure 3

7. Design a circuit to implement the truth table shown in figure 4 below. 5

Figure 4

S	R	Q	\bar{Q}
0	1	1	0
1	0	0	1
1	1	Q	\bar{Q}

 


8. A single transistor DRAM cell is represented by the circuit diagram in figure 5 below. The bit line can be precharged to $V_{DD}/2$ by using a clocked precharge circuit. Also the WRITE circuit is assumed here to bring the potential of the bit line to V_{DD} or 0V during the WRITE operation with word line at V_{DD} . Using the parameters given 8

$$V_{T0} = 1.0V$$

$$\gamma = 0.3 V^{1/2}$$

$$|2\phi_F| = 0.6V$$

Figure 5

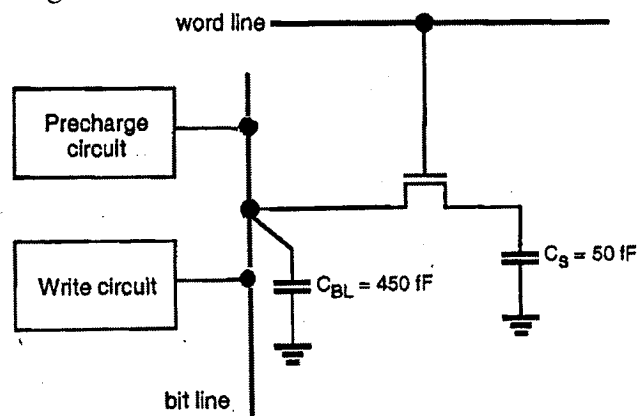

- (a) Find the maximum voltage across the storage capacitor C_S after WRITE-I operation, i.e., when the bit line is driven to $V_{DD} = 5V$.
 (b) Assuming zero leakage current in the circuit, find the voltage at the bit line during READ-operation after the bit line is first precharged to $V_{DD}/2$