

**NATIONAL INSTITUTE OF TECHNOLOGY, DELHI****Name of Examination: B. Tech (Mid-Semester September 2019)****Branch: Electrical & Electronics Engineering****Semester: V****Title of Course: Electrical Machines-II****Course Code: EEB301****Time: 2 Hrs****Maximum Marks: 25****Note: Attempt all Questions.**

Q1. Give the point answers to following questions:

- (i) Define cogging and crawling in three phase induction machine. **(2 marks)**
- (ii) Why is it preferred to place the armature winding of synchronous machine on the stator while its field winding on the rotor? **(2 marks)**
- (iii) How is the frequency transformation carried out in the rotor of three phase induction motor? **(1 marks)**

Q2. (a) Differentiate between a three phase inductor motor and a three phase synchronous motor based on the working principle. Why is the synchronous motor not self-starting **(3 marks)**(ii) Explain with proper mathematical formulation, why starting current in a three phase induction motor is low when maximum starting torque is developed. **(2 marks)**Q3. (a) Explain, with the help of neat and clear block diagram, various methods to control voltage and frequency to achieve speed control. **(2 marks)**(b) Explain the V/f method of speed control of a three phase induction motor and derive the expression of torque in terms of new and rated frequency. **(3 marks)**Q4. A three phase star connected 400 V, 50 Hz, 4-pole induction motor has the following per phase constants in ohm referred to stator  $r_1=0.15$ ,  $x_1=0.45$ ,  $r_2=0.12$ ,  $x_2=0.45$  and  $X_m=28.5$ . Fixed losses are 400 watts. Compute the stator current, rotor speed, output torque, and efficiency when the motor is operated at rated voltage and frequency at a slip of 4%. **(5 marks)**Q5. A 400 V, 1450 rpm, 50 Hz wound rotor induction motor has the following circuit model parameters:  $R_1=0.3$  ohms,  $R'_2=0.25$  ohms,  $X_1=X'_2=0.6$  ohms and  $X_m=35$  ohms. The rotational losses are 1500 watts. (a) calculate the starting torque and current when the motor is started direct on full voltage, (b) calculate the full-load current, power and net torque. **(5 marks)**

Q6. Using the Thevenin's Equivalent circuit of an Induction motor, derive the following relations neglecting the stator resistance:

$$(i) \frac{I_{2st}}{I_2} = \sqrt{\frac{s^2 + s_{mT}^2}{s^2(1 + s_{mT}^2)}} \quad (ii) \frac{I_{2.mT}}{I_2} = \sqrt{\frac{1}{2} \left[ 1 + \left( \frac{s_{mT}}{s} \right)^2 \right]}$$

where  $I_{2.st}$  is the stator load component of current at starting and  $I_{2.mT}$  is the stator load-component of current at maximum torque. **(5 marks)**

\*\*\*\*\*