

Roll No.:

National Institute of Technology, Delhi

Name of the Examination: B.Tech.

Branch : EEE, ECE

Semester : 1st

Title of the Course : IEEE

Course Code : EEB 100

Time: 2 Hours

Maximum Marks: 25

Note : 1. All the questions are compulsory. Make suitable assumptions wherever required.

2. All the symbols have their usual meaning.

Q1. In the circuit of fig. 1, find the power loss in the $1\ \Omega$ resistor by using Thevenin's theorem.

5 Marks

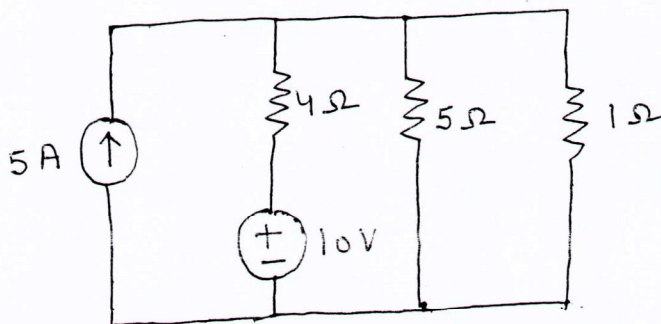


Fig. 1

Q2. In the circuit of fig. 2, find the current in $10\ \Omega$ resistor by Norton's theorem.

5 Marks

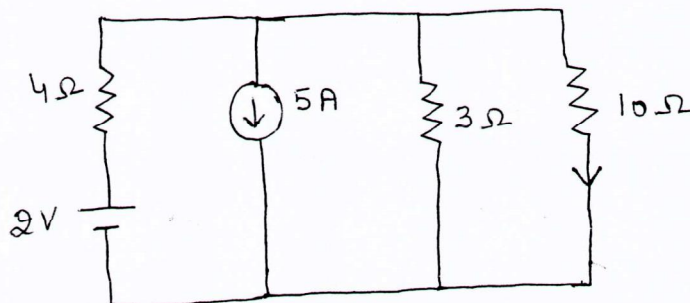


Fig. 2

Q3. a) Derive the condition for maximum power transfer across a load resistance. What is the efficiency under maximum power transfer condition?

3 Marks

b) Calculate the value of load resistance R in the circuit of fig. 3, so that maximum power is transferred to the load.

3 Marks

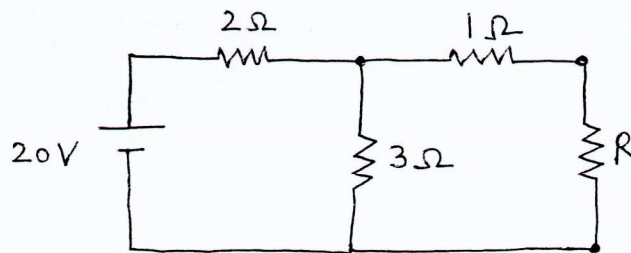


Fig. 3

Q4. For the network shown in fig. 4, calculate the equivalent resistance between nodes A and B.

4 Marks

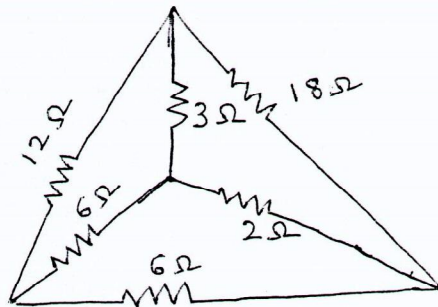


Fig. 4

Q5. Determine the current flowing in the 8 Ω resistor in the circuit shown in fig. 5 by applying Superposition theorem.

5 Marks

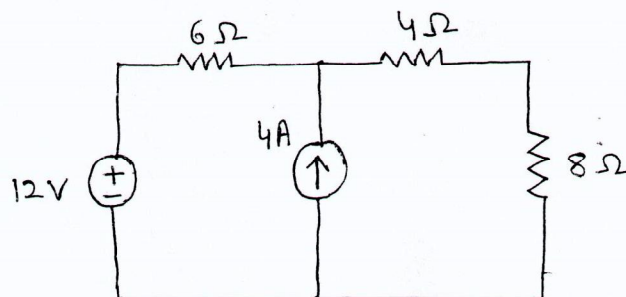


Fig 5