

Roll No.:.....

# National Institute of Technology, Delhi

Mid Semester Examination, October 2022 (B.Tech.)

Branch : ECE & EEE

Semester : V

Title of the Course : IC Applications

Course Code : ECB 304

Time : 1.5 Hours

Maximum Marks : 25


Attempt all questions. All questions carry equal marks.

(5x5)

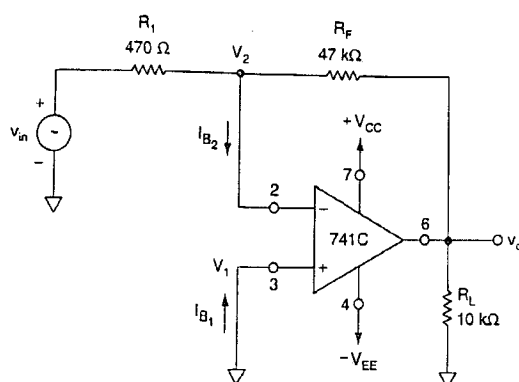- 1) (a) Draw equivalent circuit of an Opamp and its ideal voltage transfer curve.  
(b) Write short note on voltage follower using opamp.
- 2) For a non inverting amplifier (with feedback), show that the closed loop voltage gain is reduced by a factor of  $(1+AB)$ .  
Where, A is the open loop voltage gain and B is the gain of feedback loop.
- 3) What causes the gain of an op-amp to roll off after certain frequency? Derive the expression for Open loop voltage gain as a function of frequency.
- 4) (a) For the inverting amplifier given in following figure determine the maximum possible output offset voltage due to (i) Input offset voltage  $V_{io}$ . (ii) Input bias current  $I_B$ . The opamp is a type 741.  
(b) What value of Resistance ( $R_{OM}$ ) is needed to reduce the effect of input bias current  $I_B$ ?

From the 741 data sheet following values are given:

$V_{io\ max} = 6\ mV\ dc$ ,  $I_B\ max = 500\ nA\ dc$  at  $T_A = 25^\circ C$  and supply is  $+15\ (-15V)$ .



- 5) (a) Write the characteristics of practical opamp. What is the use of negative feedback in opamp circuits?  
(b) Define slew rate, input offset voltage and input bias current.