

**Aim ⇨** To design and obtain the frequency response of First Order High Pass Filter [HPF].

**Equipment Required ⇨**

Resistance, Potentiometer, Capacitor, IC 741 OP-AMP, Function Generator, CRO, Breadboard & connecting wires.

**Theory ⇨**

A high-pass filter allows signals with frequencies higher than a specified cut-off frequency  $f_L$  to pass through while attenuating frequencies lower than  $f_L$ . At the cut-off frequency, the gain of the HPF is reduced to 70.7% (or -3 dB) of its maximum value, marking the transition point between blocking and passing signals. HPFs are widely used to eliminate low-frequency noise, DC offsets, and other unwanted components from a signal.

**Roll-off Rate and Filter Order ↴**

A First Order HPF exhibits a roll-off rate of 20 dB/decade or 6 dB/octave below the cut-off frequency. This means that for every tenfold decrease in frequency, the gain decreases by 20 dB, or for every halving of frequency, the gain decreases by 6 dB. First-order filters have a gradual roll-off, making them suitable for applications where moderate attenuation of lower frequencies is acceptable.

Higher-order filters provide steeper roll-off rates, resulting in sharper cutoffs and better noise suppression but require more components and increased complexity.

**Mathematical Expression ↴**

$$f_L = \frac{1}{2\pi RC}$$

This formula derives from the basic principles of filter design, where the cut-off frequency is inversely proportional to the product of resistance and capacitance.

**Practical Considerations ↴**

The cut-off frequency is also known as the -3 dB frequency, break frequency, or corner frequency. It is a critical parameter in determining how effectively the filter can separate desired signals from unwanted low-frequency noise.

In practical applications, HPFs are used to filter out low-frequency noise from signals, ensuring that only the relevant higher-frequency components are processed. This is essential in audio processing, signal conditioning, and many other electronic applications.

## Circuit Diagram ↗

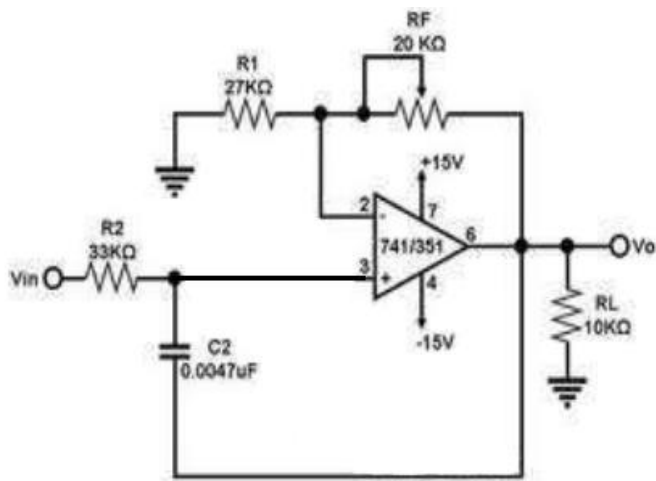


Fig. i) First Order Low Pass Filter

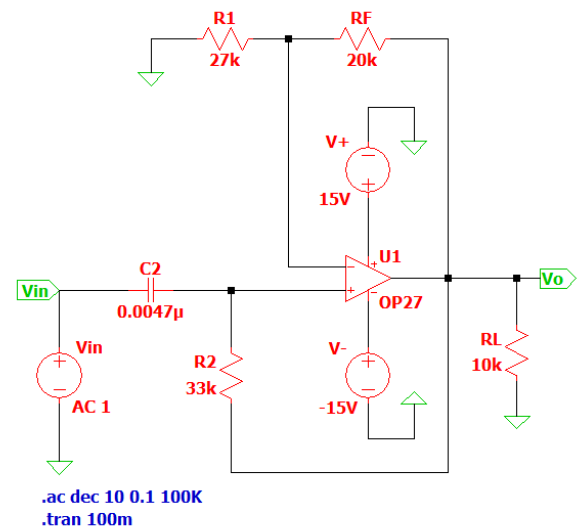


Fig. ii) LTSpice Implementation

## Observation Table ↗

### ■ Simulation Data ↗

| S.No. | Input Freq<br>f [Hz] | Gain Magnitude<br>$\left  \frac{V_o}{V_i} \right $ | Magnitude in dB<br>$20 \log \left  \frac{V_o}{V_i} \right $ |
|-------|----------------------|--|---|
| 1     | 0.1                  | 226μ   | -72.91  |
| 2     | 1                    | 2.25m  | -52.96  |
| 3     | 10                   | 23m  | -32.78  |
| 4     | 100                  | 228m   | -12.83  |
| 5     | 1K                   | 1.39   | 2.87  |
| 6     | 10K                  | 1.74   | 4.83  |
| 7     | 100K                 | 1.74   | 4.83  |

## Graphs ↗

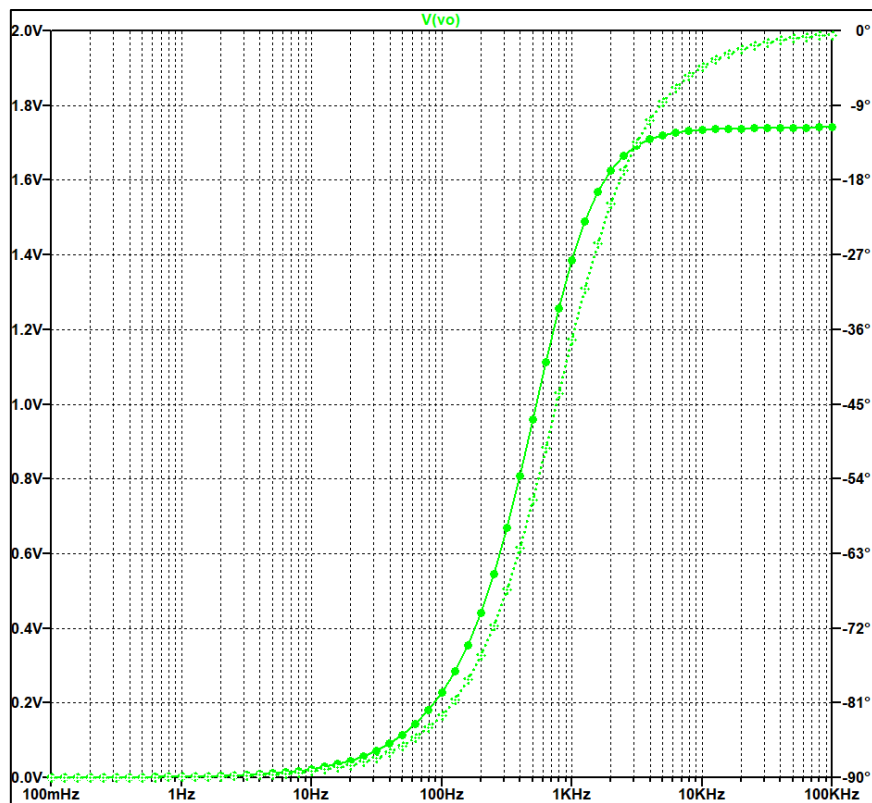


Fig. iii) Frequency Response [Linear]

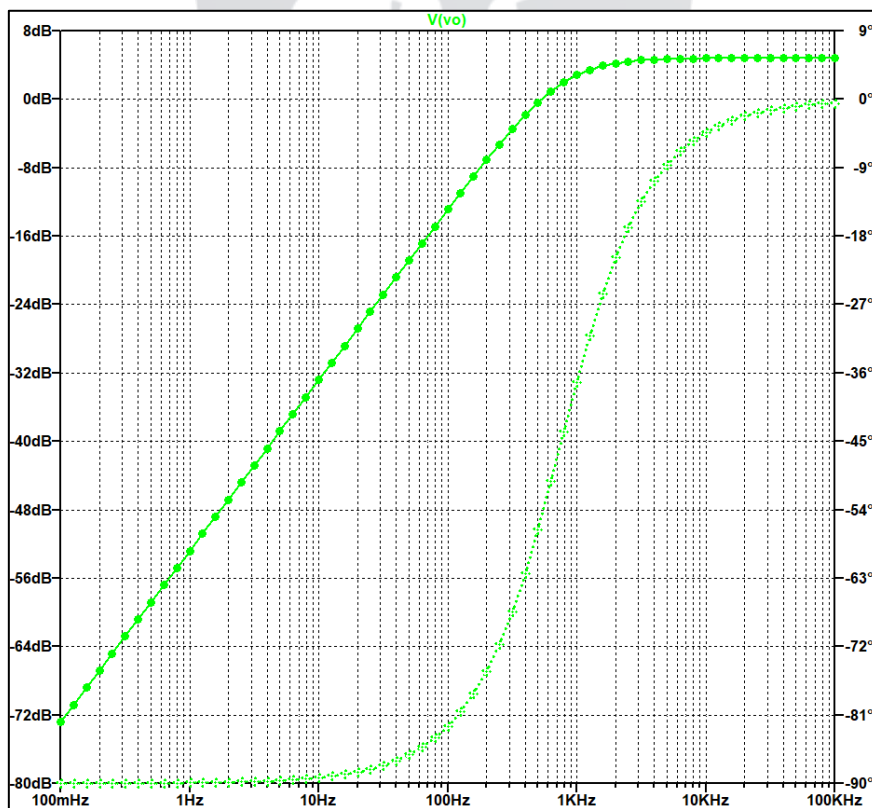


Fig. iv) Frequency Response [Decibel]

## Result ⇄

The experiment demonstrated the design and frequency response of a first-order high-pass filter. The filter passed signals above the cut-off frequency  $f_L$  and attenuated lower frequencies at 20 dB/decade, as expected.

## Conclusion ⇄

The first-order high-pass filter was designed and tested successfully, matching the expected theoretical and simulation results. The filter exhibited the correct frequency response with the predicted roll-off rate below the cut-off frequency.

## Precautions ⇄

- Ensure all connections are correct and components are securely placed.
- Do not exceed the voltage ratings of components, especially the op-amp.
- Verify capacitor polarity and op-amp orientation.
- Double-check the circuit setup before powering on the equipment.

