

Roll No.:.....

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : 5

Title of the Course : Power System Analysis

Course Code : EEL 302

Time: 3 hrs

Maximum Marks: 50

Section A

Attempt all question

(10×1 = 10)

- Q. [1] State the advantages of per unit system.
- Q. [2] For a given base voltage and base volt amperes, the per unit impedance value of an element is x . Calculate the per unit impedance value of this element when the voltage and volt amperes bases are both doubled.
- Q. [3] If the % reactance up-to the fault point is 20%, then short circuit current will be how many times of the full load current?
- Q. [4] What are the data required for load flow study.
- Q. [5] What is the need for short circuit studies?
- Q. [6] Distinguish between symmetrical and unsymmetrical faults with neat sketch.
- Q. [7] Write the symmetrical components of a three phase system?
- Q. [8] What is sequence operator?
- Q. [9] Define swing curve. What is the use of this curve?
- Q. [10] Define transient stability of a power system

Section B

Attempt any four

(4×5 = 20)

- Q. [1] What do you understand by percentage reactance? Why do we prefer to express the reactances of various elements in percentage values for short-circuit calculations?
- Q. [2] Derive and explain the equal area criterion for stability of a power system.
- Q. [3] Explain the step by step procedure of load flow solution for the Fast Decoupled Load Flow (FDLF) method.
- Q. [4] Three zones of a single phase circuit are identified in the following Fig. A. The zones are connected by transformer T_1 and T_2 , whose rating are also shown. Given $V_s = 220\angle 0^\circ$, $X_{line} = 2\Omega$ and $Z_{load} = (0.9 + j0.2)$. Using base values of 30 kVA and 240 volts in zone 1, draw the per-unit impedance circuit and the per unit source voltage. Also calculate the load current both in per-unit and in amperes. Transformer winding resistances and shunt admittance branches are neglected.

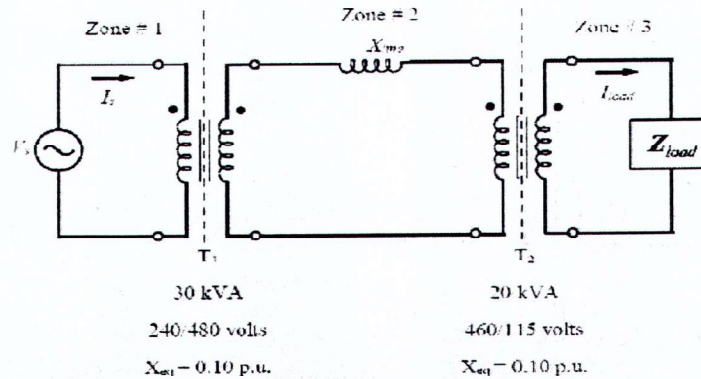


Fig. A

- Q. [5] A 3-phase transmission line operating at 10 kV and having a resistance of 1 ohm and reactance of 4 ohm is connected to the generating bus-bars through 5 MVA step-up transformer having a reactance of 5%. The bus-bars are supplied by a 10 MVA alternator having 10% reactance. Calculate the short-circuit current, if it occurs, (i) at the load end of transmission line, (ii) at the high voltage terminals of the transformer in fig. B.

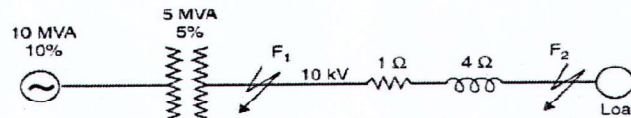


Fig. B

Section C

Attempt any two

(2×10 = 20)

- Q. [1] Derive swing equation and discuss the importance of stability studies in power system planning and operation.
- Q. [2] **Figure C** shows the one-line diagram of a simple three-bus power system with generation at buses 1 and 3. The voltage at bus 1 is $V_1 = 1.025 \angle 0^\circ$. Voltage magnitude at bus 3 is fixed at 1.03 p.u. with a real power generation of 300 MW. A load consisting of 400 MW and 200 MVAR is taken from bus 2. Line impedances are marked in per unit on a 100 MVA base and line charging susceptances are neglected. Obtain the power flow solution by the Gauss-Seidel method up-to the first iteration. Determine the line flows and line losses. Construct a power flow diagram showing the direction of line flow.

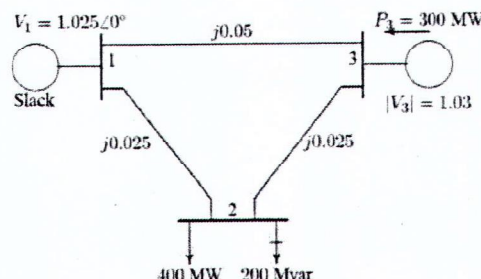


Figure: C

- Q. [3] Make the Jacobian matrix for network shown in **figure C**. What will be the matrix size of Jacobian and their sub-matrix J_1, J_2, J_3 and J_4 ? Also, write the step-wise solution procedure of power flow using Newton-Raphson method for **figure C**.