



## NATIONAL INSTITUTE OF TECHNOLOGY DELHI

Make-up Examination July 2017

Year- II

Name of Specialization: EEE

Semester: 3<sup>rd</sup> / 5<sup>th</sup>

Course Name: Analog Electronics

M.Marks:50

Course Code: EC 220

Time : 3.00 Hrs.

Q.1. Given the load line of Fig.1 and the defined Q-point, determine the required values of  $V_{CC}$ ,  $R_C$ , and  $R_B$  for a fixed-bias configuration. 6 marks

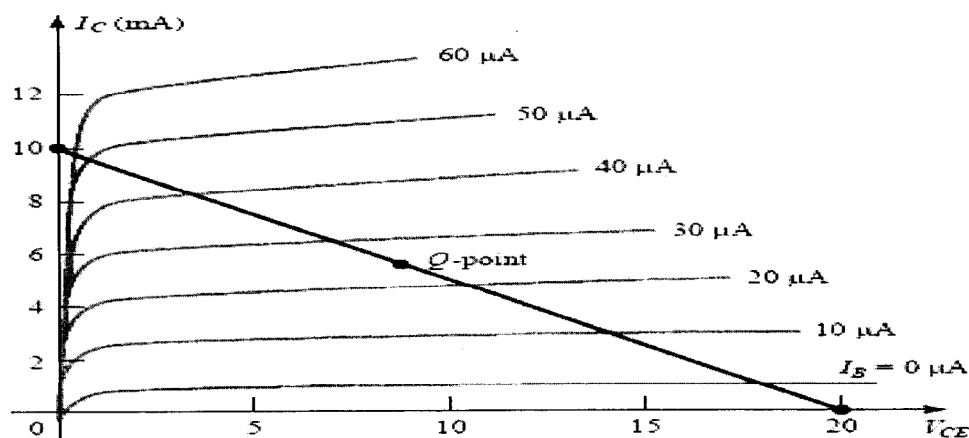


Fig.1

Q.2. Describe various methods used for transistor biasing with the help of circuit diagram. 6 marks

Q.3. Given  $I_E = 2.5$  mA,  $h_{fe} = 140$ ,  $h_{oe} = 20$   $\mu$ S ( $\mu$ mho), and  $h_{ob} = 0.5$   $\mu$ S, determine:

(a) The common-emitter hybrid equivalent circuit.

(b) The common-base  $r_e$  model

(4+4) marks

Q.4. Discuss different types of power amplifiers. Show that maximum collector efficiency of class B power amplifier is 78.5%. (5+3) marks

Q.5. What improvements can be obtained using negative feedback? Explain the effect of negative feedback on gain and bandwidth. Derive an expression of input resistance in voltage-series feedback amplifier. (2+2+2) marks

Q.6. Explain the criterion for oscillation. Draw the circuit diagram of we in bridge oscillator and explain its operation. (2+4) marks

Q.7. Draw the schematic block diagram of the basic Op-Amp with inverting and non-inverting inputs. List six characteristics of the ideal operational amplifier. 5 marks

Q.8 Explain with the help of circuit diagram, the operation of a stable **OR** mono stable multi vibrator. 5 marks