

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch

: ECE

Semester

: V

Title of the Course

: Linear Integrated Circuits

Course Code


: EC 303

Time: 2 Hours


Maximum Marks: 30

- Note: Question 1 carries 65 questions 2 mark each. Rest questions 2 to 7 carries 3 marks each.
- Questions are printed on BOTH sides. Answers should be CLEAR, TO THE POINT AND LEGIBLE.
- All parts of a single question must be answered together and in the same sequence as given in question paper. ELSE QUESTION SHALL NOT BE EVALUATED.

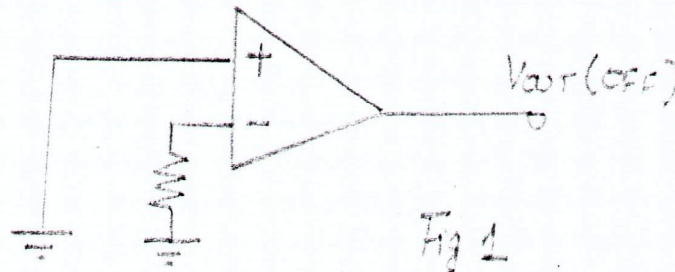
- Q1. (a) An OPAMP has a differential gain of 10^3 and a CMRR of 100. What will be the output voltage of the OPAMP with inputs $120 \mu\text{V}$ and $80 \mu\text{V}$? [2]
- (b) Using the frequency scaling technique, convert the 1 KHz cutoff frequency of low pass filter to a cutoff frequency of 1.6 KHz. [2]
- (c) A 100 pF capacitor has a maximum charging current of $150 \mu\text{A}$. What will be its slew rate? [2]
- (d) For the given circuit of fig. 1, $I_{in(off)} = 20 \text{ nA}$. If $V_{in(off)} = 0 \text{ V}$, what is the differential input voltage? What will be the output offset voltage? [2]



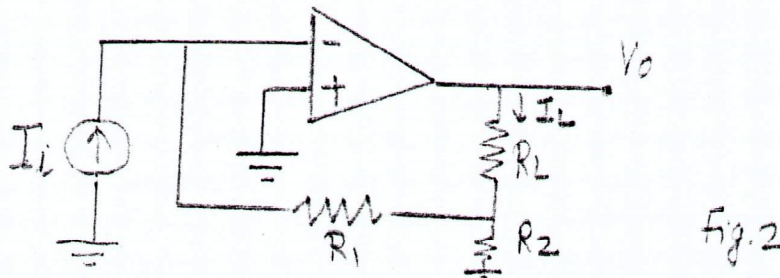- (e) For the current converter shown in fig. 2, prove that $\frac{I_L}{I_i} = -(1 + \frac{R_1}{R_2})$. [2]




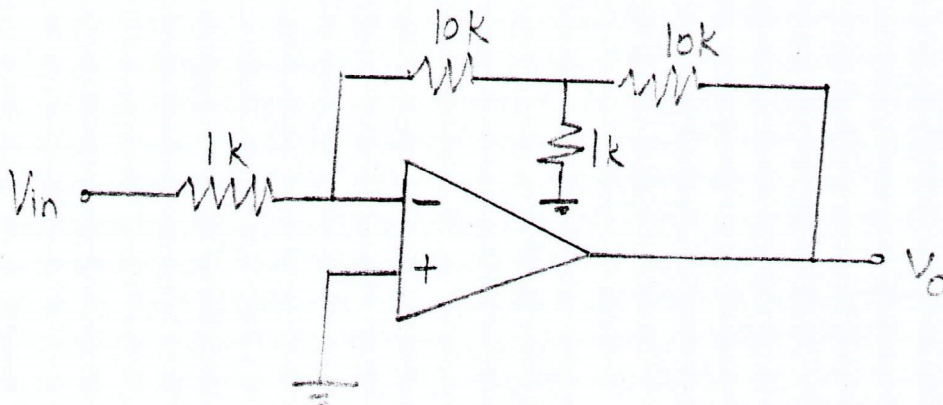- (f) Assuming the OPAMP to be ideal, what will be the gain for the circuit of fig. 3. [2]




- Q 2. (a). Verify that the circuit shown in fig. 4 has input impedance $\frac{V_i}{I_i} = \frac{R_1 R_2}{Z}$.
 (b). If Z is a capacitor, show that the system behaves as an inductor.
 (c). Find the value of C in order to obtain a 1H inductance if $R_1 = R_2 = 1K$.

[3]

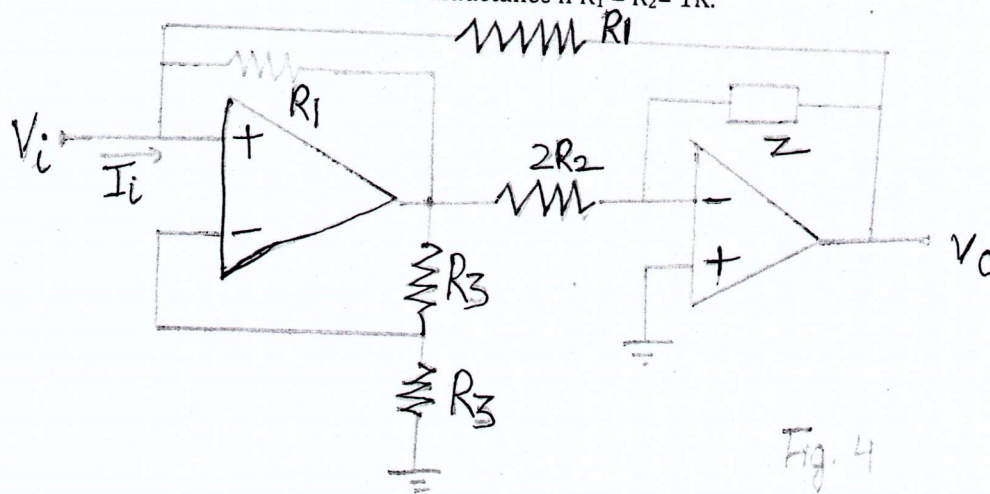


- Q 3. For the differential amplifier shown in fig. 5, verify that $v_o = -\left(1 + \frac{2R_2}{R_3}\right) \frac{R_f}{R_1} (v_x - v_y)$.

[3]

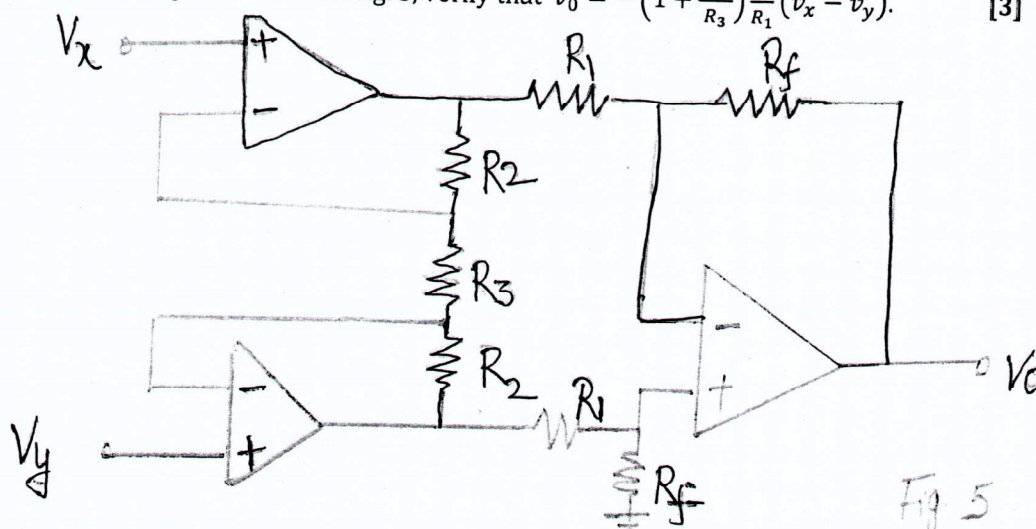

- Q 4. Determine the output voltage in each of the following cases for the differential amplifier of fig. 6,
 (a) $v_{in1} = 5mVdc$, $v_{in2} = -7\mu Vdc$ (b) $v_{in1} = 10mVrms$, $v_{in2} = 20mVrms$
 Specifications of the OPAMP are given below:
 $A = 200,000$, $R_i = 2M\Omega$, $R_o = 75\Omega$, $+V_{CC} = +15V$, $-V_{EE} = -15V$, and voltage swing $= \pm 14V$.

[3]

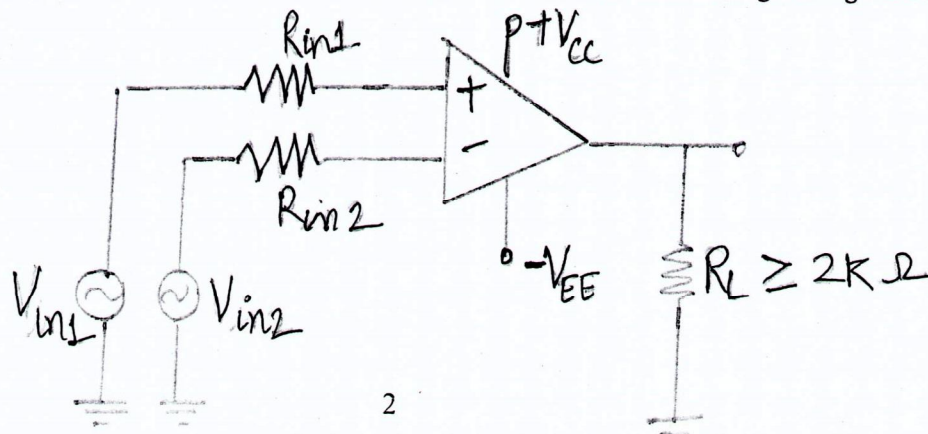

Q 5. Design a switched capacitor integrator for $f_0 = 10 \text{ Hz}$. Compare the values with an RC integrator. [3]

Q 6. For the circuit shown in fig. 7, if the input is a constant V , show that the output is given by a differential equation. [3]

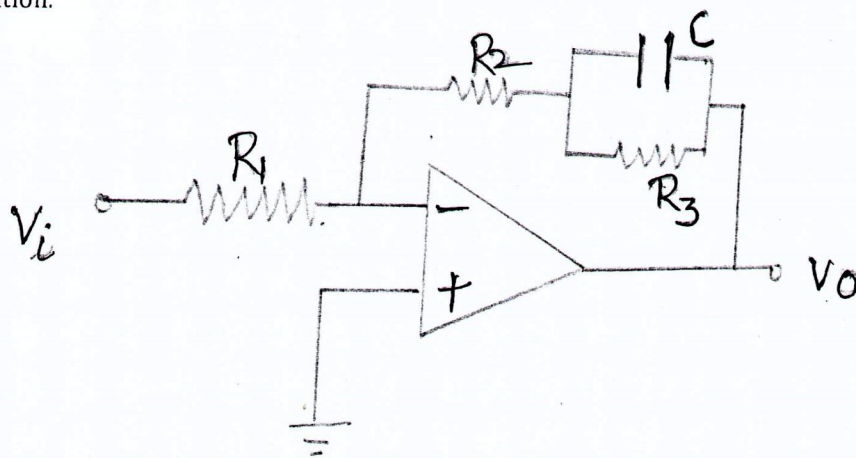


Fig. 7

Q 7. Find out the transfer function of the circuits given in fig. 8. [3]

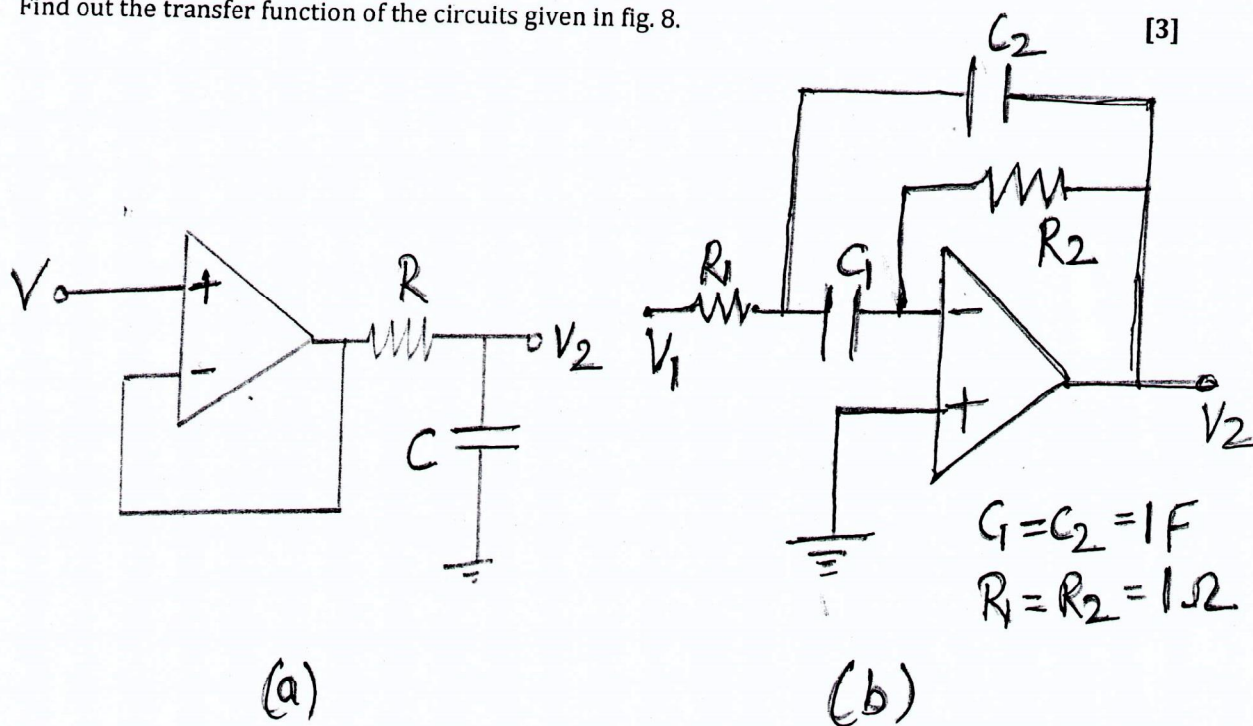


Fig. 8