

Roll No.:.....

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE/ECE

Semester : 3rd

Title of the Course : Network analysis and synthesis

Course Code : EEL 201

Time: 3 Hours

Maximum Marks: 50

Section A (Answer all questions)

10×1=10

1. (i) According to Millman's theorem, if there are n voltage source with n internal resistances respectively, are in parallel the value of equivalent voltage is _____.

- (ii) Draw the pole zero diagram of given function


$$F(s) = \frac{2s + 1}{(s - 1)(s^2 - 8s + 15)}$$

- (iii) State the reciprocity theorem.

- (iv) Draw complete phasor diagram of voltages and currents in star connection.

- (v) Power in 3ph balanced system is measured by two wattmeter method. The load is operating at 0.5 lagging power factor. What will be the reading of 2 wattmeters?

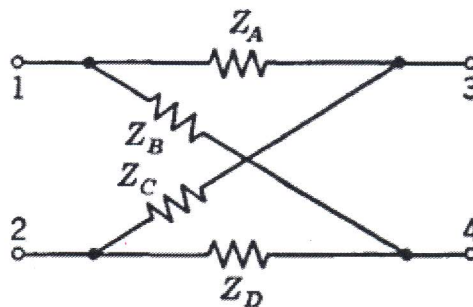- (vi) Find the Z parameter of the following lattice network.



- (vii) What are the possible locations of poles for pure L-C network?

- (viii) Check the polynomial is Hurwitz or not

$$s^4 + s^3 + 2s^2 + 3s + 2$$

- (ix) What are the condition for reciprocity and symmetry for ABCD parameter?


- (x) If $F(s) = \frac{P(s)}{Q(s)} = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$, M being even part and N being odd part, then write the condition for positive realness of $F(s)$.

Section B (Answer any four question)

4×5=20


2. The star-connected load having impedance of $(12-j16) \Omega$ per phase is connected in parallel with the delta-connected load having impedance of $(27+18j) \Omega$ per phase with both the loads being balanced, and fed from a three-phase, 230 V, balanced delta connected supply, with the phase sequence as RYB. Find the line current and power factor.

[5]

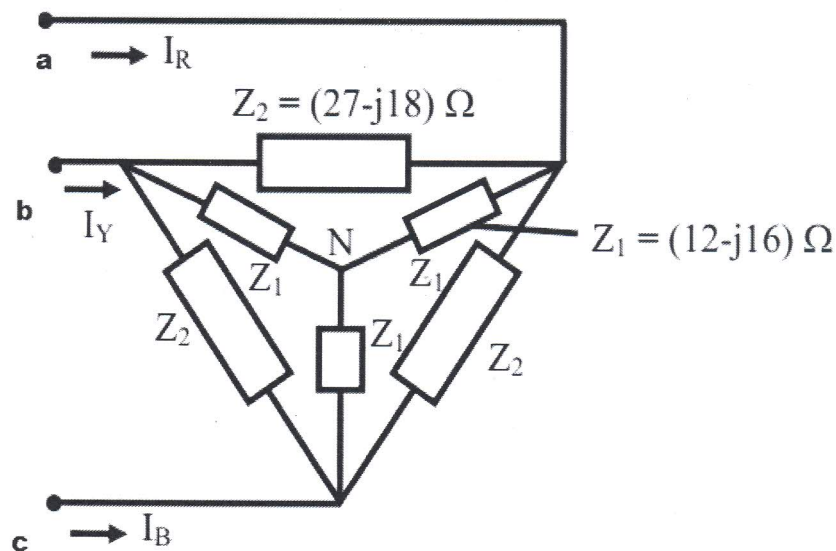


3. The unbalance delta load is supplied by Delta connected balanced voltage of 200V in positive sequence. Find the line currents and the total power drawn by the load.

[5]

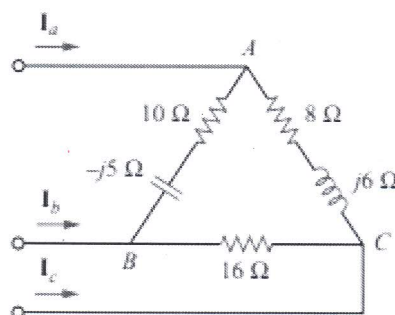


4. Find out the current through each branch of following network and hence comment on Tellegen's theorem.

[5]

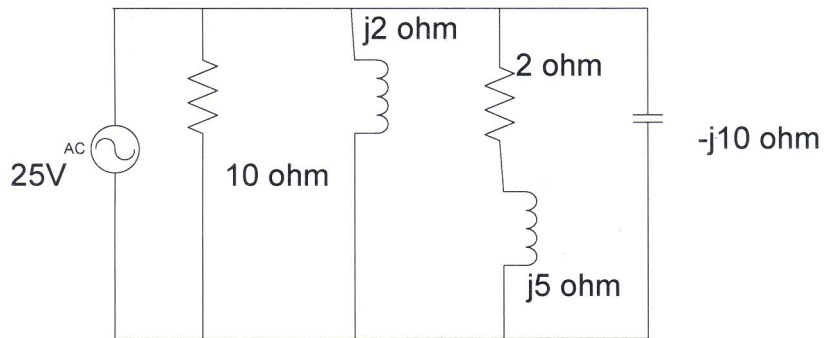


5. Find out transmission parameter of the following network.

[5]

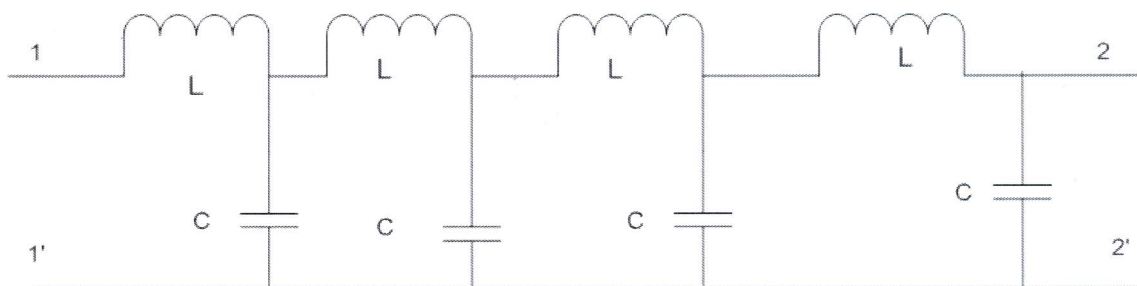

6. Find out the voltage transfer function of given circuit.

[5]

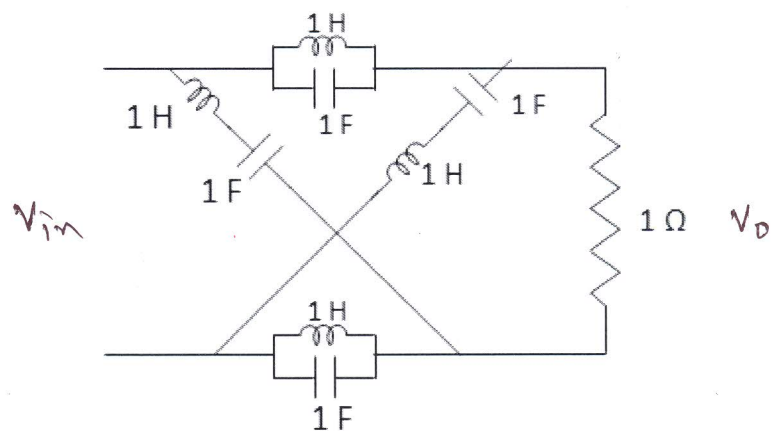

Section C (Answer any two question)

10×2=20

7. The driving point functions of one port is given by

[10]

$$z(s) = \frac{8(s^2 + 4)(s^2 + 25)}{s(s^2 + 16)}$$

Synthesis the given function in Foster 1st and 2nd form.

8. Driving point function is given by

[10]

$$F(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

Synthesis the function in Cauer 1st and 2nd method.

9. a. Find the limits of K so that the following polynomial is a Hurwitz

[5]

$$s^4 + 25s^3 + 15s^2 + 20s + K$$

- b. What are the significance of positive real function and Hurwitz polynomial in network synthesis.

[5]

.....END.....