

Roll No.....

## National Institute of Technology Delhi

Name of the Examination: B.Tech

Branch : EE & ECE

Semester : III

Course Name : Network Analysis & Synthesis

Course Code : EEL-201

Time: 2:00 hour

Maximum Marks: 25

Note:

- All Questions are compulsory.
- Do not write irrelevant theory.
- Assume data where ever required.

Q1) For the network shown in Fig. 1, determine the y-parameters.

(4)

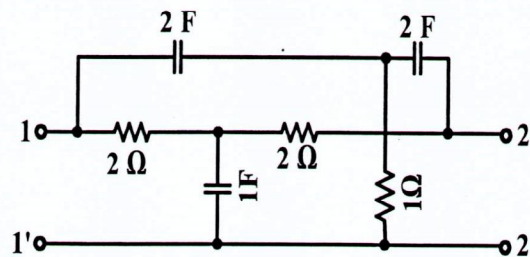


Fig.1

Q2) The h – Parameters of a Two – Port Network shown in the figure – 2 are  $h_{11} = 1000\Omega$ ;  $h_{12} = 0.003$ ;  $h_{21} = 100$ ;  $h_{22} = 50 \times 10^{-6} \text{ mho}$ . Find  $V_2$  and Z – Parameters of the network if  $V_s = 10^{-2} \angle 0^\circ \text{ V}$ .

(4)

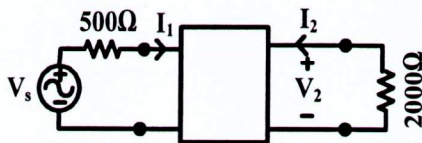


Fig. 2

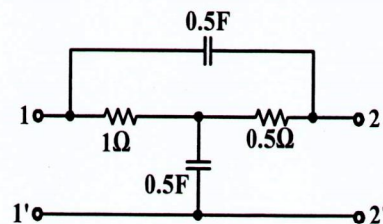


Fig. 3

Q3) For the bridge-T network as shown in fig-3, find the y-parameters and its equivalent  $\Pi$ - network. (4)

Q4) Determine the y and z-parameters for the network shown in fig-4.

(4)

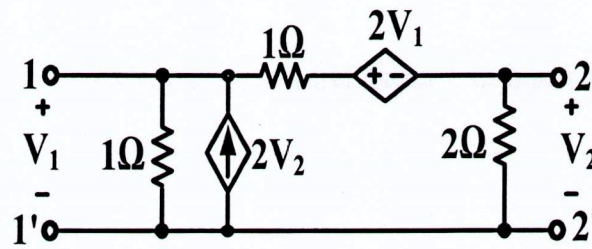


Fig-4

Q5) Express h-parameters in terms of y-parameters and ABCD-parameters of a two port network.

(4)

Q6) Find the driving point impedance at the terminals 1-1' of the ladder network as shown in fig-5.

(3)

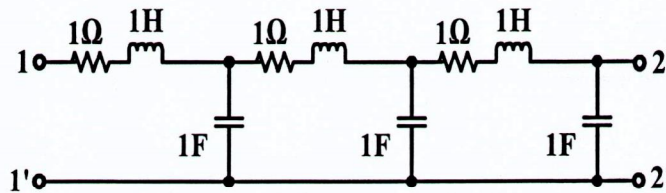


Fig-5

Q7) What are the advantages of polyphase systems over single-phase systems?

(2)