

National Institute of Technology, Delhi

Name of the Examination: Mid Semester Examination (Autumn Semester 2022)

Branch : ECE

Semester : 3rd

Title of the Course : Digital Electronics

Course Code : ECB 202

Time: 1.5 Hours

Maximum Marks: 25

Note: All questions are compulsory.

Section A: Answer all the questions. Each question carries 5 marks.

[5×5=25]

- A1. a) Obtain the reduced POS expression from given minterms
 $\sum m(2,3,6,7,10,11,12,14)$ using K-Map. [5]
b) Obtain the reduced SOP expression from given minterms
 $\sum m(0,2,4,5,6,7,8,10,13,15)$ using K-Map
- A2. a) Design and implement Half Subtractor showing all designing steps. [5]
Difference (D) = A XOR B Borrow (B) = A'B
b) Design a Full Subtractor using the above-designed Half Subtractor
- A3. a) Design a multiplexer for given function $f(A,B,C,D) = \sum m(1,2,4,7,8,11,13,14)$ [5]
with 3 select lines.
b) Implement a full adder using a 3:8 decoder.
- A4. Design a 4-bit Binary to BCD code converter. [5]

Section B: Answer any one

[5×1=5]

- B1. Design a 4-bit BCD Adder and explain its working with the help of a suitable example.
- B2. Design and explain carry look-ahead adder with the help of a suitable example.

***** All The Best *****