

Roll No.:

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : IV

Title of the Course : Digital Electronics and Logic Design Course Code : CSB 254

Time: 3 Hours

Maximum Marks: 50

Note:

- Answers should be CLEAR, TO THE POINT AND LEGIBLE.
- All parts of a single question must be answered together. ELSE QUESTION SHALL NOT BE EVALUATED.
- All questions in Section A are compulsory. Attempt any 4 questions from Section B and 2 questions from Section C.

Section A

- Q 1 Solve the following problems (1×10)
- Convert the decimal number 11.35 into equivalent octal number.
 - Find 15's and 16's complement of hexadecimal number (ABCD)₁₆.
 - Show that NOR gate is a universal gate.
 - A clock of frequency 120MHz is being applied to cascaded stages of MOD-4 and MOD-3 counters. What will be the frequencies at the output of MOD-4 and MOD-3 counters, respectively?
 - Verify the following Boolean expression using Boolean algebra:
 $AB + AC + B\bar{C} = AC + B\bar{C}$.
 - Simplify the given function $f(A, B, C, D) = \sum(3, 4, 5, 7, 9, 13, 14, 15)$, using K-map.
 - An equality detector gives the output $y = 1$, if both the inputs A and B are either 1 or 0. Construct the truth table and obtain the Boolean expression for y .
 - Implement the XOR function using NOR gate.
 - Find all the prime implicants for the Boolean function $F(w, x, y, z) = \sum(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$, and determine which are essential?
 - In a 4-bit Johnson ring counter, if propagation delay of each flip-flop is 10 ns, then calculate the maximum frequency that can be applied to the counter.

Section B

- Q 2 Reduce the expression and implement the same using OAI implementation (5)
- $$F(A, B, C, D) = \prod(2, 8, 9, 10, 11, 12, 14)$$
- Q 3 Write the count sequence of a 4-bit binary up counter. Design a synchronous series carry counter using flip-flop for this sequence. Also, draw the waveforms of outputs with clock signal. (5)
- Q 4 Implement $F(A, B, C) = \sum(0, 2, 4, 6, 7)$ using two stage 2×1 MUX. (5)

Q 5 Draw the circuit diagram of 4-bit Ring counter using JK-FF. Explain its working with suitable timing diagrams. (5)

Q 6 What is full subtractor? Obtain the expression for difference and borrow output from truth table. Implement the logic circuit using two half-subtractor. (5)

Section C

Q 7 (a) Draw a 4-bit look ahead carry adder along with designing equations and explanations. (5)

(b) Implement a full adder circuit using two 4×1 multiplexers. (5)

Q 8 (a) What is race-around condition? Explain, how this can be eliminated? (5)

(b) Implement SR-FF using T-FF. (5)

Q 9 Explain the following programmable logic devices with suitable diagram (10)

- a. ROM
- b. PROM
- c. PLA
- d. PAL

-End of the paper-