

National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : ECE

Semester : IV

Title of the Course : ANALOG ELECTRONICS

Course Code : ECB 206

Time: 3 Hours

Maximum Marks: 50

- Answers should be CLEAR AND TO THE POINT. All parts of a single question must be answered together. ELSE QUESTION SHALL NOT BE EVALUATED.

1. A p-n-p Ge transistor is used in the self-biasing arrangement given in figure 1, where $V_{CC}=4.5\text{ V}$, $R_C=1.5\text{ K}\Omega$, $R_E=0.27\text{ K}\Omega$, $R_2=2.7\text{ K}\Omega$, $R_1=27\text{ K}\Omega$ and $|V_{BE}|=0.2\text{ V}$. If $\beta=44$, find: [1+2+2]
(a) The stability factor, S (b) the Q-point, (c) recalculate these values (S and Q-pt) if the base spreading resistance of $690\text{ }\Omega$ is taken into consideration.
2. In the Darlington stage, shown in figure 2, $V_{CC}=24\text{ V}$, $\beta_1=24$, $\beta_2=39$, $V_{BE}=0.6\text{ V}$, $R_C=330\text{ }\Omega$ and $R_E=120\text{ }\Omega$. If at the Q-point of second transistor, $V_{CE2}=6\text{ V}$, determine (a) resistance value, R, (b) stability factor 'S' defined as $S=dI_C/dI_{C01}$. [5]
3. Consider second collector to first emitter feedback pair configuration in figure 3. Calculate (a) A_{v1} (b) A_{v2} (c) A_v (d) β (e) A_{v_f} (f) R_o (g) R_{of} and (h) R_{if} for the amplifier configuration. Assume, $R_s=0$, $h_{fe}=50$, $h_{ie}=1.1\text{ K}$, $h_{re}=h_{oe}=0$ and all transistors are identical. [8x2]
4. The transistor in following figure 4, is connected as CE amplifier and the h-parameters are given in the following table. If $R_s=R_L=1\text{ K}\Omega$, find (a) A_v (b) A_{vs} (c) A_i and (d) A_{is} . [4]

Parameters	Values
$h_{11}=h_i$	$1100\text{ }\Omega$
$h_{12}=h_r$	2.5×10^{-4}
$h_{21}=h_f$	50
$h_{22}=h_o$	$25\text{ }\mu\text{A/V}$
$1/h_o$	40 K

5. Show that the overall h parameters of the accompanying two-stage cascaded amplifier, shown in figure 5, are: [5]
 (a) $h_{11}=h_{11}'-\frac{h_{12}'h_{21}'}{1+h_{22}'h_{11}''}h_{11}''$ (b) $h_{12}=\frac{h_{12}'h_{12}''}{1+h_{22}'h_{11}''}$
 (c) $h_{21}=\frac{h_{21}'h_{21}''}{1+h_{22}'h_{11}''}$ (d) $h_{22}=h_{22}''-\frac{h_{12}''h_{21}'}{1+h_{22}'h_{11}''}h_{22}'$
6. Write true (T)/ false (F) against each statement. [10x0.5]
 (a) Compensation circuits refer to resistive biasing circuits.
 (b) Negative feedback is more suitable for amplification.

- (c) Tentatively Q-point for a self-bias circuit will be at the middle of load line.
 - (d) Q-point should be fixed with $V_{CEQ} < V_{CC}/2$ in order to avoid thermal runaway.
 - (e) The term low frequency implies the range of frequencies of the input signal in which effects of internal capacitances are considered.
 - (f) CC amplifier provides current gain instead of voltage gain.
 - (g) A CE transistor stage connected in series with a CB transistor stage provides the cascode combination.
 - (h) Difference amplifier is used to amplify the difference between two signals.
 - (i) At α -cut off frequency, the high frequency α falls to $0.707 \alpha_0$.
 - (j) At high frequency operation, h-parameters are real numbers.
7. Write brief notes on followings: [2+2]
- (a) CB physical model of transistor with early feedback generator and base spreading resistance.
 - (b) Transistor two port device and hybrid model.
8. Opt for the correct option only. [6x1]
- (a) In a self-bias circuit, the stability increases, as the base resistance **increases/decreases/ remains constant**.
 - (b) An amplifier supplies output current proportional to the signal voltage and independent of R_s and R_L known as- **trans-resistance/ trans-conductance/ current** amplifier.
 - (c) Physical model of transistor includes **early feedback generator/base spreading resistance /both**.
 - (d) Operation of feedback network is **unidirectional/bi-directional/omni-directional**.
 - (e) For an oscillator, the source of electrical input is **D.C. supply/ac source/generated noise**.
 - (f) From a circuit design point of view, more practical parameter to measure **transistor gain/transistor gain with feedback/transistor gain with feedback and including source**.
-