

# National Institute of Technology, Delhi

Name of the Examination: B. Tech.

End Semester Examination (Autumn, 2019)


Branch : ECE and EEE Semester : 3<sup>rd</sup>  
 Title of the Course : Network Analysis and Synthesis Course Code : EEL 201

Time: 3 Hours


Maximum Marks: 50

## SECTION A: ANSWER ALL QUESTIONS

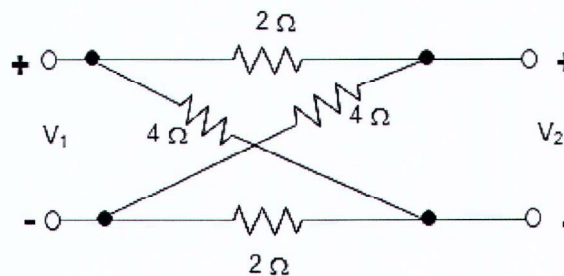1. What are the conditions of reciprocity and symmetry for ABCD-parameters and h-parameters? (1)
2. The power drawn by a three-phase induction motor is measured using two wattmeter method. The readings of wattmeter  $W_1$  and  $W_2$  are 10 kW and 5 kW respectively. Calculate the total three-phase real power and total three-phase reactive power. (1)
3. Determine the Z-parameters for the following circuit. (1)



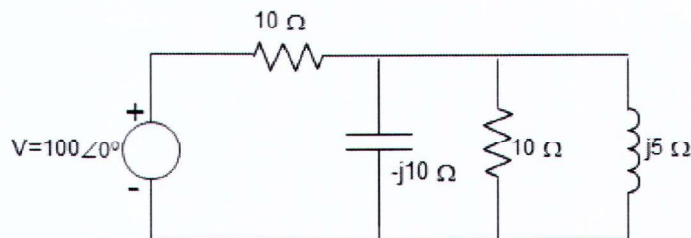
4. State Reciprocity theorem and Millman's theorem. (1)
5. Draw the phasor diagram for the voltage and currents in delta connection and give the relation between line current and phase current and line voltage and phase voltage. (1)
6. Find the active power delivered by the source in the circuit given below: (1)



7. What are the restrictions on the location of poles and zeros in the driving point functions? (1)
8. Write all the equivalent Y-parameters for two parallel connected 2-port network and draw its equivalent circuit. (1)

9. Obtain the transfer function of the given network:

(1)

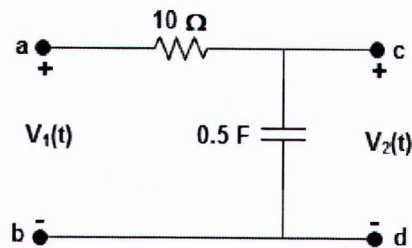


10. Using Routh-Hurwitz criterion, determine the range of values of a system parameter  $K$  for which the system is stable.  $F(s) = s^3 + 3s^2 + 3s + K = 0$

(1)

### SECTION B: ANSWER ANY FOUR QUESTION

11. Determine the  $Y$  parameters and  $Z_{out}$  for the terminated two port network given as follows:

(5)

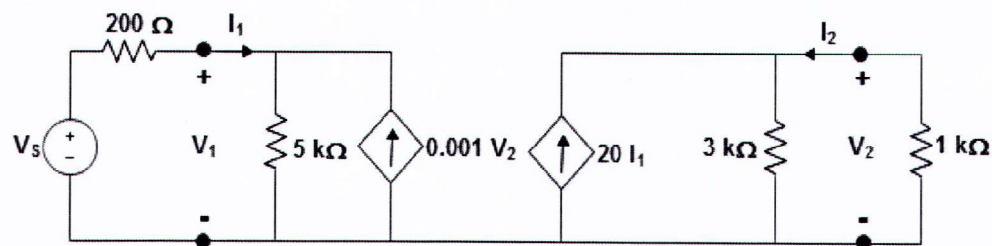


12. Check whether the following function is the positive real function or not with the proper justification.

$$F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

(5)

13. Determine the driving point impedance, transfer impedance, transfer admittance, voltage transfer ratio and current transfer ratio for the circuit given below.


(5)

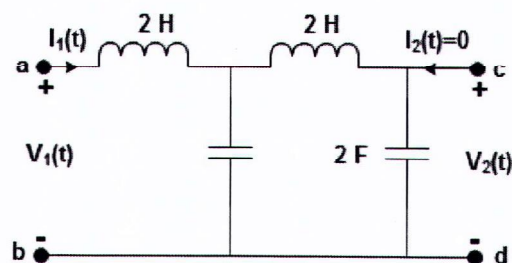

14. A balanced three phase 400 V supply is applied across the lines of a delta connected load having a parallel combination of resistance and capacitance in each phase. The resistance and capacitive reactance values are  $5 \Omega$  and  $-j5 \Omega$  respectively. Determine the phase current and line current in each phase and draw the phasor diagram. (5)
15. Comment whether the following polynomials are Hurwitz polynomial or not with the proper justification. (a)  $F(s) = s^5 + 3s^4 + 3s^3 + 4s^2 + s + 1$  (b)  $F(s) = s^4 + s^3 + 2s^2 + 4s + 1$  (5)

### SECTION C: ANSWER ANY TWO QUESTION

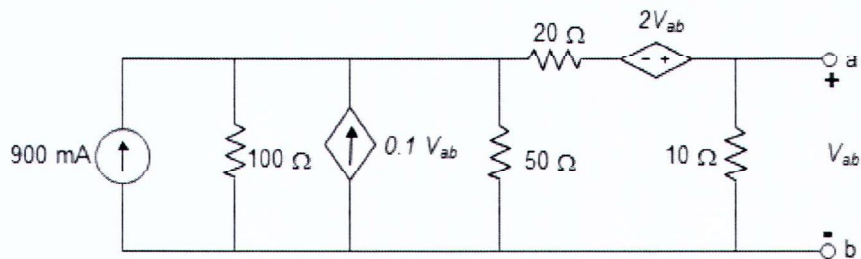16. Determine the Thevenin and Norton equivalents of the given circuit across the terminals a and b. Also, determine the value of the resistance that would absorb maximum power from the given circuit when connected across the terminals a and b and calculate the maximum power. (10)



17. Show that the driving point function,  $Z(s)$  can be realized in both the Cauer-I and Cauer-II forms

of networks. 
$$Z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$
 (10)

18. A three phase induction motor takes 100 kVA at 0.6 pf (lagging) from a 440 V, 50 Hz balanced three phase source. Another delta connected load which is having the series combination of resistance value of  $8 \Omega$  and reactance value of  $-j 24 \Omega$  in each phase is connected to the same source. Determine the total active power, total reactive power, total VA power, line current and the power factor of the combination. (10)