

Roll No.:.....

# National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : Electrical & Electronics Engg.

Semester : 6<sup>th</sup>

Title of the Course : Switch Gear and Protection

Course Code : EEL 352

Time: 2 Hours

Maximum Marks: 25


Note : 1. Answer all the questions.

2. Each question carries 5 marks.

4. Do not write anything on the question paper except Roll number

1. Explain the scheme and working of wheatstone bridge type negative and zero sequence relay.
2. Explain the construction and working of Reactance and Mho relays. What are the disadvantages of each relay.
3. Derive the torque equation of directional relay. Explain any one directional over current relay connection used for three phase systems.
4. Explain solid, resistance and Peterson coil grounding schemes.
5. Figure shows a radial distribution system having identical IDMTL over-current relay at A, B and C. For a time delay step of 0.5 second, Calculate the time multiplier settings at A and B

PSM	2	3	5	10	20
Time (seconds)	10	6	4.5	3	2

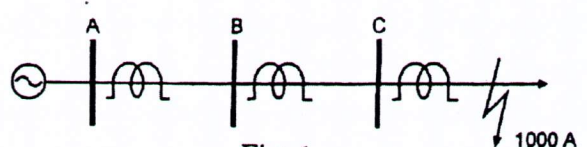

C T Ratios	200/5	200/5	100/5
Plug setting current	5 A	2.5 A	2.5 A
Time multiplier setting	—	—	0.1