

Roll No.:.....

National Institute of Technology, Delhi

Name of the Examination: B.Tech.

Mid Semester Examination (Spring, 2023)

Branch : ECE Semester : IVth
 Title of the Course : Electronics Measurement & Instrumentation Course Code : ECB 254

Time: 1 Hour 30 Minutes

Maximum Marks: 25

Note: All questions are compulsory.

COURSE OUTCOMES		COGNITIVE LEVELS
CO1	Analyze instrument characteristics, errors and generalized measurement system.	Understanding (Level II)
CO2	Analyze and use the circuit for the measurement of R, L, C, F, I, V etc	Analyzing (Level IV)
CO3	Use of Ammeters, Voltmeter and Multimeters and CRO for measurement	Evaluating (Level V)
CO4	Analyze and interpret different signal generator circuits for the generation of various waveforms with the use of different display devices and recorders	Analyzing (Level IV)

Course Outcomes (CO's)	CO1	CO2
Questions No.	Q1, Q2, Q3	Q4, Q5 & Q6

Answer the following questions.

- Q1.** Define the Accuracy and Precision within application? An $820\ \Omega$ resistance with an accuracy of $\pm 10\%$ carries a current of 10 mA. The current was measured by an analog ammeter on a 25 mA range with an accuracy of $\pm 2\%$, of full scale. Calculate the power dissipated in the resistor, and determine the accuracy of the result. **[3Marks]**
- Q2.** The expected value of the voltage across a resistor is 80 V. However, the measurement gives a value of 79 V. Calculate (i) absolute error, (ii) % error (iii) relative accuracy, and (iv) % of accuracy. **[3 Marks]**
- Q3.** By using a "micrometer screw", the following readings were taken of a certain physical length: 1.34, 1.38, 1.56, 1.47, 1.42, 1.44, 1.53, 1.48, 1.40, and 1.59 all are in mm. calculate the following; (i) Arithmetic mean, (ii) Average deviation (iii) Standard deviation, and (iv) Variance. **[4 Marks]**
- Q4.** Identify the bridge used for measurement of inductance and explain the **[5 Marks]**

construction and operation of this bridge. In the AC bridge circuit shown in Fig. 1, the supply voltage is 20 V at 500 Hz. Arm **ab** is $0.25 \mu\text{F}$ pure capacitance; arm **bc** is 400Ω pure resistance and arm **ad** has a 120Ω resistance in parallel with a $0.15 \mu\text{F}$ capacitor. Find resistance and inductance or capacitance of the arm **cd** considering it as a series circuit.


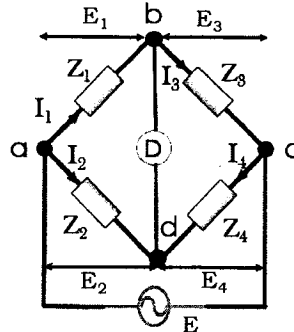


Fig.1 A. C. Bridge

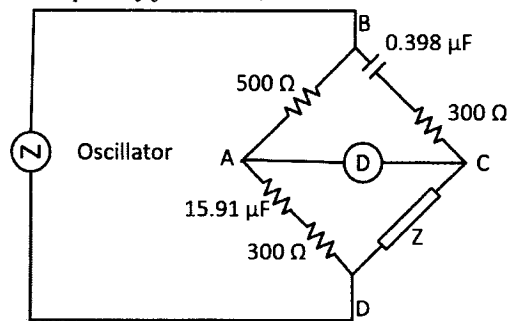- Q5.** Explain how a Maxwell bridge can be used for measuring an unknown inductance. [5 Marks]
The bridge shown in the figure is used to measure the impedance Z . If the bridge is balanced for oscillator frequency $f=2 \text{ KHz}$, then Find the value of impedance Z .



- Q6.** A Schering bridge is operated on 800 V with a frequency of 500 Hz in order to measure a high voltage capacitor. The following data is given about the balanced bridge $C_1 = 0.2 \mu\text{F}$, $C_3 = 2200 \text{ pF}$, $R_3 = 1.5 \text{ k}\Omega$, and $R_4 = 12 \text{ k}\Omega$. [5 Marks]
Determine : (a) value of unknown capacitor (b) dissipation factor (c) Draw the phasor diagram.