

Library 9/3/18  
(Evening)

Roll No.: .....

# National Institute of Technology, Delhi

Name of the Examination: B. Tech

Branch : EEE

Semester : 4

Title of the Course : Power Systems

Course Code : EEL 253

Time: 02 Hrs

Maximum Marks: 25

Note: Attempt all questions.

Mark

- Q. [1] What is single line diagram? 2
- Q. [2] How are the loads represented in reactance or impedance diagram? 2
- Q. [3] A single-phase voltage source with  $V = 100 \angle 130^\circ$  volts delivers a current  $I = 10 \angle 10^\circ$  A. Calculate the source real and reactive power and state whether the source delivers or absorbs each of these. 4
- Q. [4] Two loads connected in parallel are supplied from a single-phase 240-V rms source. The two loads draw a total real power of 400 kW at a power factor of 0.8 lagging. One of the loads draws 120 kW at a power factor of 0.96 leading. Find the complex power of the other load. 4
- Q. [5] Prove that star connected circuit impedance is equivalent to one third of delta connected circuit impedance i.e.  $Z_Y = \frac{Z_\Delta}{3}$ . 4
- Q. [6] Evaluate the transmission line A, B, C, D parameter for nominal  $\pi$  (pi) method. 4
- Q. [7] A 3-phase, 50 Hz overhead transmission line 100 km long with 132 kV as line voltage at the receiving end. The line has following constants: (i) Resistance = 0.17 ohm/km/phase, (ii) Inductance = 1.1 mH per km/phase, (iii) Capacitance = 0.0082 micro-farad per km/phase. Using nominal T-method find voltage, current, power factor of the sending end when 70 MW at 0.8 p.f. lagging load is connected at receiving end. 5