

Roll No :

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE and CSE

Semester : III

Title of the Course : Analog Electronics

Course Code : ECB-206

Time: 3 Hrs

Maximum Marks: 50

Section A: Answer the 10 multiple choice questions. Each question carries 01 mark.


[10×1=10]

- A1. Ripple factor of half wave rectifier is
a) 1.414 b) 1.21 c) 1.3 d) 0.48
- A2. Component that eliminates fluctuations in rectified voltage and produces a relatively smooth DC voltage is
a) rectifier b) Modulator c) Filter d) Amplifier
- A3. When transistors are used in digital circuits they usually operate in the:
a) active region b) breakdown region c) saturation and cutoff regions d) linear region
- A4. A current ratio of I_C/I_E is usually less than one and is called:
a) beta b) theta c) alpha d) Omega
- A5. Power amplifier directly amplifies
a) Voltage of signal b) Current of the signal c) Power of the signal d) All of the mentioned
- A6. JFET is a _____ carrier device.
a) Unipolar b) Bipolar c) Minority d) Majority
- A7. In an oscillator if phase of feedback is same as that of oscillation waveform then feedback is called _____
a) Positive feedback b) Negative feedback c) Cannot be predicted d) Either positive or negative depending upon frequency
- A8. Which of these is incorrect for an operational amplifier?
a) It has a high voltage gain b) It is a direct coupled amplifier
c) It is only useful for amplifying AC signals d) It was originally designed to perform mathematical operations
- A9. Which of the following configuration is used for impedance matching?
a) Common base configuration b) Common emitter configuration
c) Common collector configuration d) All configurations are equally suited
- A10. Which of the following correctly determines the relation between α and β ?
a) $\beta = \alpha / (1 - \alpha)$ b) $\alpha = \beta / (1 - \alpha)$ c) $\beta = \alpha / (1 - \beta)$ d) $\beta = \alpha * (1 - \beta)$

Section B: Answer any 4 questions. Each question carries 05 mark.

[4×5=20]

- B1. Discuss the classification of power amplifiers and explain the working of Class-A amplifier with suitable circuit diagram and waveform.
- B2. Explain how LC tank circuit is used to generate AC oscillations in an electronic oscillator and what is the condition for oscillation?
- B3. Explain in detail the concept of Virtual Ground in operational amplifiers (Op-Amp) and discuss any 4 parameters of Op-Amp.
- B4. In a transistor Hartley oscillator, if $L_1 = 0.1 \text{ mH}$, $L_2 = 10 \text{ } \mu\text{H}$ and mutual inductance between the two coils $M = 20 \text{ } \mu\text{H}$, calculate the value of capacitor C_1 of oscillatory circuit to obtain frequency of 4110 KHz.
- B5. For the circuit shown below, determine DC output voltage, PIV and Rectification efficiency.

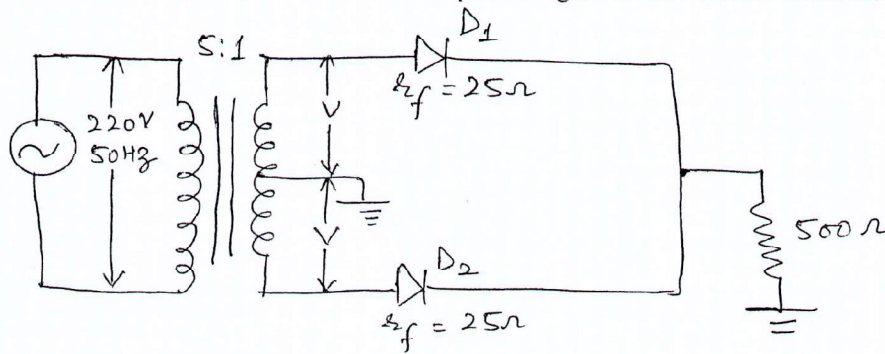

Section C: Answer any 2 questions. Each question carries 10 mark.

[2×10=20]

- C1. Explain the need of h-parameters. Draw the h-parameter equivalent circuit for common emitter configuration and derive input impedance, current gain, voltage gain and output admittance for the same?
- C2. Distinguish between FET and BJT. Explain the construction and working principle of FET with the help of suitable diagrams. Also explain Drain characteristics in detail.
- C3. Write a short note on any **Two** of the following:
 - a) Avalanche and Zener Breakdown
 - b) Clipper and Clamper Circuit
 - c) Voltage divider biasing circuit