

National Institute of Technology, Delhi

Name of the Examination: B. Tech.

Branch : EEE and ECE.

Semester : 1stTitle of the Course : Introduction to Electrical &
Electronics Engineering

Course Code : EEB100

Time: 2 Hours

Maximum Marks: 25

Note : 1. This paper contains 6 questions in 2 printed pages.

2. Answer all the questions.

3. Do not write anything on the question paper except Roll number

1. A battery of 2V and negligible internal resistance is connected between terminals A and C of the Wheatstone bridge as shown in Fig. 1. A galvanometer of $40\ \Omega$ resistance is connected between B and D. Determine the magnitude and direction of current in the galvanometer using Thevenin's theorem. [3]

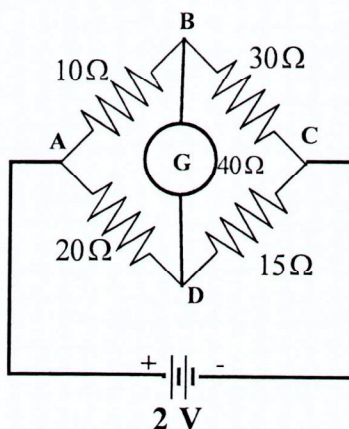


Fig. 1

2. Using delta/star transformation, find the galvanometer current in the Wheatstone bridge shown in Fig.1. [4]

3. Determine the Norton's equivalent between the terminals X and Y of Fig. 2.

[5]

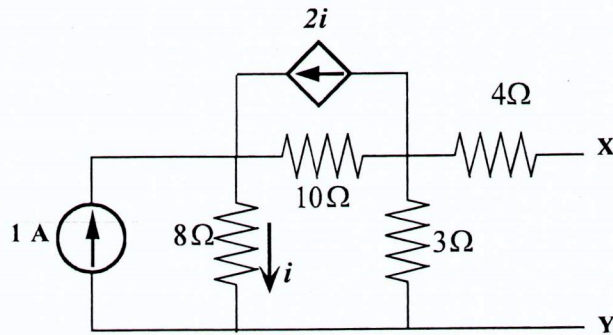


Fig. 2

4. A resistance R , an inductance $L=0.01\text{ H}$ and a capacitance C are connected in series. When an alternating voltage $v=400\sin(3000t-20^\circ)$ is applied to the series combination, the current flowing is $10\sqrt{2}\sin(3000t-65^\circ)$. Find the values of phase angle, R and C . [4]
5. (a) Derive the equations for resonant frequency and Q-factor of a series resonance circuit,
 (b) Derive the equations for resonant frequency, Q-factor and circuit impedance at resonance of a practical parallel resonance circuit. [2+3]
6. A balanced three phase system supplies an unbalanced delta load made up of 2 resistances of $100\ \Omega$ and $200\ \Omega$ and a coil having an inductance of 0.3 H with negligible resistance. The line to line voltage is 100 V and supply frequency is 50 Hz . Calculate (a) Total Active power in the system, and (b) total reactive volt amperes. [4]